


EXP 3: DESIGN OF 8-TO-3 ENCODER (WITHOUT AND WITH PRIORITY)

AIM: Design of 8-to-3 encoder (without and with priority) using HDL code.


SOFTWARE & HARDWARE:

1. XILINX VIVADO 2018.1 VERSION.
2. FPGA-ZYNQ BOARD **XC7Z020CLG484-1**.
3. JUMPER CABLE WITH POWER SUPPLY.

8:3 encoder Block diagram:

 

8:3 encoder logic Diagram :

 

Digital Inputs								Binary Output		
D7	D6	D5	D4	D3	D2	D1	D0	X	Y	Z
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

Truth Table of 8:3 encoder

VERILOG CODE :


Structural Model	Data Flow Model
<pre> module encoder (din, dout); input [7:0] din; output [2:0] dout; reg [2:0] dout; Or g1(dout[0],din[1],din[3],din[5],din[7]); Or g2(dout[1],din[2],din[3],din[6],din[7]); Or g3(dout[2],din[4],din[5],din[6],din[7]); Endmodule </pre>	<pre> module encoder (din, dout); input [7:0] din; output [2:0] dout; reg [2:0] dout; Assign=dout[0],din[1],din[3],din[5],din[7]); Or g2(dout[1],din[2],din[3],din[6],din[7]); Or g3(dout[2],din[4],din[5],din[6],din[7]); Endmodule </pre>

BehaviouralModel	BehaviouralModel with Enable
<pre> module encoder (din, dout); input [7:0] din; output [2:0] dout; reg [2:0] dout; always @(din) begin if (din ==8'b00000001) dout=3'b000; else if (din==8'b00000010) dout=3'b001; else if (din==8'b00000100) dout=3'b010; else if (din==8'b00001000) dout=3'b011; else if (din==8'b00010000) dout=3'b100; else if (din ==8'b00100000) dout=3'b101; else if (din==8'b01000000) dout=3'b110; else if (din==8'b10000000) dout=3'b111; else dout=3'bX; end endmodule </pre>	<pre> module encwtoutprio(a,en,y); input [7:0] a; input en; output reg [2:0] y; always@(a or en) begin if(!en) y<=1'b0; else case(a) 8'b00000001:y<=3'b000; 8'b00000010:y<=3'b001; 8'b00000100:y<=3'b010; 8'b00001000:y<=3'b011; 8'b00010000:y<=3'b100; 8'b00100000:y<=3'b101; 8'b01000000:y<=3'b110; 8'b10000000:y<=3'b111; endcase end endmodule </pre>


TEST BENCH

```
module encodert_b;  
reg [0:7] d;  
wire a;  
wire b;  
wire c;  
encodermdu uut (.d(d), .a(a), .b(b),.c(c) );  
initial begin  
#10 d=8'b10000000;  
#10 d=8'b01000000;  
#10 d=8'b00100000;  
#10 d=8'b00010000;  
#10 d=8'b00001000;  
#10 d=8'b00000100;  
#10 d=8'b00000010;  
#10 d=8'b00000001;  
#10 $stop;  
end  
endmodule
```

 
Simulation output: Waveform window: Displays output waveform for verification.



8:3 Priority encoder Block diagram:

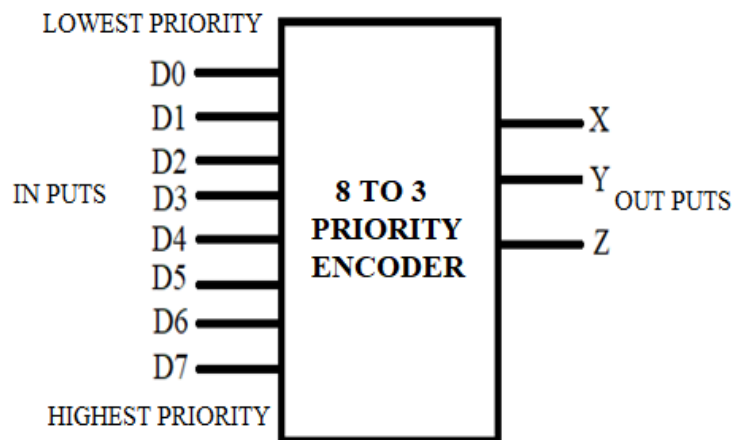

8:3 Priority encoder logic Diagram :

 

Digital Inputs								Binary Output		
D7	D6	D5	D4	D3	D2	D1	D0	X	Y	Z
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	X	0	0	1
0	0	0	0	0	1	X	X	0	1	0
0	0	0	0	1	X	X	X	0	1	1
0	0	0	1	X	X	X	X	1	0	0
0	0	1	X	X	X	X	X	1	0	1
0	1	X	X	X	X	X	X	1	1	0
1	X	X	X	X	X	X	X	1	1	1

Truth Table of 8:3 encoder

VERILOG CODE :

Structural Model	Data Flow Model
<pre>module prior_otb_enco(DOUT, D); output [2:0] DOUT; input [7:0] din; wire din7_not, din6_not, din5_not, din4_not, din2_not; wire wa0, wa1, wa2, wa3, wa4;; //instantiate gates not g0 (din7_not, din[7]), g1 (din6_not, din[6]), g2 (din5_not, din[5]), g3 (din4_not, din[4]), g4 (din2_not, din[2]); and g5 (wa0, din6_not, din4_not, din[3]), g6 (wa1, din5_not, din4_not, din[3]), g7 (wa2, din5_not, din4_not, din[2]),</pre>	<pre>module prio_enco_8x3(dout, din); output [2:0] dout; input [7:0] din ; assign dout = (din[7] ==1'b1) ? 3'b111: (din[6] ==1'b1) ? 3'b110: (din[5] ==1'b1) ? 3'b101: (din[4] ==1'b1) ? 3'b100: (din[3] ==1'b1) ? 3'b011: (din[2] ==1'b1) ? 3'b010: (din[1] ==1'b1) ? 3'b001: (din[0] ==1'b1) ? 3'b000: 3'bxxx; endmodule</pre>

```

    g8 (wa3, din6_not, din[5]),
    g9  (wa4,   din6_not,   din4_not,
din2_not, din[1]);
    or   g11(dout[2], din[7], din[6], din[5],
din[4]),
    g12(dout[1], din[7], din[6], wa1, wa2),
    g13(dout[0], din[7], wa0, wa3, wa4),
    g14(V, din[0], din[1], din[2], din[3],
din[4], din[5], din[6], din[7]);
endmodule


```

BehaviouralModel	BehaviouralModel with Enable
<pre> module encoder (din, dout); input [7:0] din; output [2:0] dout; reg [2:0] dout; always @(din) begin if (din ==8'b00000001) dout=3'b000; else if (din==8'b0000001 X) dout=3'b001; else if (din==8'b000001 XX) dout=3'b010; else if (din==8'b00001XXX) dout=3'b011; else if (din==8'b0001XXXX) dout=3'b100; else if (din ==8'b001XXXXX) dout=3'b101; else if (din==8'b01XXXXXX) dout=3'b110; else if (din==8'b1XXXXXXX) dout=3'b111; else dout=3'bX; end endmodule </pre>	<pre> module priori (en,din,dout); input en; input [7 : 0] din; output [2 : 0] dout; reg [2 : 0] dout; always@(en,din) begin if(en == 1) // Active high enable begin dout = 3'bZZZ; // Initializing dout to high Impedance end else begin casex(din) 8'b00000001 :dout = 3'b000; 8'b0000001X :dout = 3'b001; 8'b000001XX :dout = 3'b010; 8'b00001XXX :dout = 3'b011; 8'b0001XXXX :dout = 3'b100; 8'b001XXXXX :dout = 3'b101; 8'b01XXXXXX :dout = 3'b110; 8'b1XXXXXXX :dout = 3'b111; endcase end end endmodule </pre>

Test Bench Code :

```
module prio_enco_8x3_tst;
  reg [7:0] d_in;
  wire[2:0] d_out;
  prio_enco_8x3 u1 (.d_out(d_out), .d_in(d_in) );
  initial
    begin
      d_in=8'b11001100; #10;
      d_in=8'b01100110; #10;
      d_in=8'b00110011; #10;
      d_in=8'b00010010; #10;
      d_in=8'b00001001; #10;
      d_in=8'b00000100; #10;
      d_in=8'b00000011; #10;
      d_in=8'b00000001; #10;
      d_in=8'b00000000; # 10;
      $stop;
    end // initial begin
endmodule
```

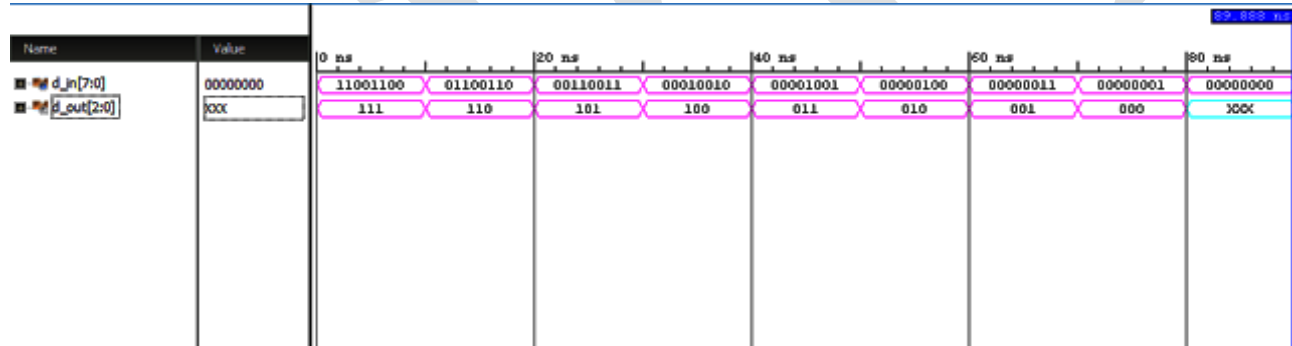Simulation output: Waveform window: Displays output waveform for verification.



RESULT:

Thus the OUTPUT of 8 to 3 decoder (without and with priority) is verified by simulating the VERILOG HDL code.