

Chapter 5:

Chapter 5. Gate-level Modeling

5.4 Exercises

1. Create your own 2-input Verilog gates called `my_or`, `my_and` and `my_not` from 2-input Nand gates. Check the functionality of these gates with a stimulus module.

My answer:

```
1 //exercise my own gates
2
3 module my_gates(c1,c2,c3,a,b);
4   output c1,c2,c3;
5   input a,b;
6
7   //my_or
8   wire a1,b1;
9   nand (a1,a,a);
10  nand (b1,b,b);
11  nand my_or (c1,a1,b1);
12
13  //my_and
14  wire e;
15  nand (e,a,b);
16  nand my_and(c2,e,e);
17
18  //my_not
19  nand my_not(c3,a,a);
20
21  endmodule
```

```

1 //stimulus
2 module stimulus;
3 reg a,b;
4 wire c1,c2,c3;
5
6 initial
7 begin
8     a=1'b0; b=1'b0;
9     #10 a=1'b0; b=1'b1;
10    #10 a=1'b1; b=1'b0;
11    #10 a=1'b1; b=1'b1;
12 end
13
14 my_gates m1(c1,c2,c3,a,b);
15
16 initial
17 begin
18     $monitor($time, "a= %b, b= %b, c1= %b,
19             c2= %b, c3= %b\n",a,b,c1,c2,c3);
20 end
21
22 endmodule

```

```

0a= 0, b= 0, c1= 0,
  c2= 0, c3= 1

10a= 0, b= 1, c1= 1,
  c2= 0, c3= 1

20a= 1, b= 0, c1= 1,
  c2= 0, c3= 0

30a= 1, b= 1, c1= 1,
  c2= 1, c3= 0

```

2. A 2-input xor gate can be built from my_and, my_or and my_not gates. Construct an xor module in Verilog that realizes the logic function, $z=xy'+x'y$. Inputs are x and y, and z is the output. Write a stimulus module that exercises all four combinations of x and y inputs.

My answer:

```

1 //exercise 2.
2 module my_xor(z,x,y);
3 output z;
4 input x,y;
5
6 wire x_n,y_n,x_ny,xy_n;
7
8 //~x , ~y
9 my_gates m1(.c3(x_n),.a(x));
10 my_gates m2(.c3(y_n),.a(y));
11
12 //~xy, x~y
13 my_gates m3(.c2(x_ny),.a(x_n),.b(y));
14 my_gates m4(.c2(xy_n),.a(x),.b(y_n));
15
16 //z
17 my_gates m5(.c1(z),.a(x_ny),.b(xy_n));
18
19 endmodule

```

```

1 //stimulus
2 module stimulus;
3 reg x,y;
4 wire z;
5
6 initial
7 begin
8     x=1'b0; y=1'b0;
9     #10 x=1'b0; y=1'b1;
10    #10 x=1'b1; y=1'b0;
11    #10 x=1'b1; y=1'b1;
12 end
13
14 my_xor x1(z,x,y);
15
16 initial
17 begin
18     $monitor($time, "x= %b, y= %b, z= %b\n", x,y,z);
19 end
20
21 endmodule

```

```

0x= 0, y= 0, z= 0
10x= 0, y= 1, z= 1
20x= 1, y= 0, z= 1
30x= 1, y= 1, z= 0

```

3. The 1-bit full adder described in the chapter can be expressed in a sum of products form.

$sum = a.b.c_{in} + a'.b.c_{in}' + a'.b'.c_{in} + a.b'.c_{in}'$

$c_{out} = a.b + b.c_{in} + a.c_{in}$

Assuming a,b,c_in are the inputs and sum and c_out are the outputs, design a logic circuit to implement the 1-bit full adder, using only and, not ,and or gates. Write the Verilog description for the circuit. You may use up to 4-input Verilog primitive and and or gates. Write the stimulus for the full adder and check the functionality for all input combinations.

my answer:

```

1 //exercise 3, 1-bit full adder
2 module fa(a,b,c_in,sum,c_out);
3 output sum,c_out;
4 input a,b,c_in;
5
6 wire s1,s2,s3,s4; //s1=abc_in, s2=a'bc_in', s3=a'b'c_in, s4=ab'c_in'
7 wire a_n,b_n,c_in_n;
8 wire c1,c2,c3; //c1=ab, c2=bc_in, c3=ac_in
9
10 not (a_n,a);
11 not (b_n,b);
12 not (c_in_n,c_in);
13
14 and (s1,a,b,c_in);
15 and (s2,a_n,b,c_in_n);
16 and (s3,a_n,b_n,c_in);
17 and (s4,a,b_n,c_in_n);
18 and (c1,a,b);
19 and (c2,b,c_in);
20 and (c3,a,c_in);
21
22 or (sum,s1,s2,s3,s4);
23 or (c_out,c1,c2,c3);
24
25 endmodule

```

```

1  //stimulus
2  module test;
3  reg a,b,c_in;
4  wire sum,c_out;
5
6  fa f1(a,b,c_in,sum,c_out);
7
8  initial
9  begin
10     a=1'b0;b=1'b0;c_in=1'b0;
11     #10 a=1'b0; b=1'b0; c_in=1'b1;
12     #10 a=1'b0; b=1'b1; c_in=1'b0;
13     #10 a=1'b0; b=1'b1; c_in=1'b1;
14     #10 a=1'b1; b=1'b0; c_in=1'b0;
15     #10 a=1'b1; b=1'b0; c_in=1'b1;
16     #10 a=1'b1; b=1'b1; c_in=1'b0;
17     #10 a=1'b1; b=1'b1; c_in=1'b1;
18  end
19
20  initial
21  begin
22     $monitor($time, "a= %b, b= %b, c_in= %b, c_out= %b, sum= %b\n",a,b,c_in,c_out,sum);
23  end
24
25  endmodule


```

```

0a= 0, b= 0, c_in= 0, c_out= 0, sum= 0
10a= 0, b= 0, c_in= 1, c_out= 0, sum= 1
20a= 0, b= 1, c_in= 0, c_out= 0, sum= 1
30a= 0, b= 1, c_in= 1, c_out= 1, sum= 0
40a= 1, b= 0, c_in= 0, c_out= 0, sum= 1
50a= 1, b= 0, c_in= 1, c_out= 1, sum= 0
60a= 1, b= 1, c_in= 0, c_out= 1, sum= 0
70a= 1, b= 1, c_in= 1, c_out= 1, sum= 1

```

 4. The logic diagram for an RS latch with delay is shown below.



Write the Verilog description for the RS latch. Include delays of 1 unit when instantiating the nor gates. Write the stimulus module for the RS latch, using the following table, and verify the outputs.

set	reset	q_{n+1}
0	0	q_n
0	1	0
1	0	1
1	1	?

My answer:

```

1 //exercise 4, sr latch
2 module sr_latch(r,s,q,qb);
3   input r,s;
4   output q,qb;
5
6   nor #(1) n1(q,r,qb);
7   nor #(1) n2(qb,s,q);
8
9   endmodule

```


```

1 //stimulus
2 module test;
3   reg r,s;
4   wire q,qb;
5
6   sr_latch m1(.r(r),.s(s),.q(q),.qb(qb));
7
8   initial
9   begin
10      s=1'b0; r=1'b0;
11      #10 s=1'b0; r=1'b1;
12      #10 s=1'b1; r=1'b0;
13      #10 s=1'b1; r=1'b1;
14   end
15
16   initial
17   begin
18      $monitor($time, " s= %b, r= %b, q= %b\n", s,r,q);
19   end
20
21   endmodule

```



 5. Design a 2-to-1 multiplexer using buif0 and buif1 gates as shown below.



The delay specification for gates b1 and b2 are as follows:

	<i>Min</i>	<i>Typ</i>	<i>Max</i>
Rise	1	2	3
Fall	3	4	5
Turnoff	5	6	7

Apply stimulus and test the output values.

My answer:

```

1 //exercise 5, mux2-to-1
2 module mux2_to_1(out,in1,in0,s);
3 output out;
4 input in1,in0,s;
5
6 buif1 #(1:3:5,2:4:6,3:5:7) b2(out,in1,s);
7 buif0 #(1:3:5,2:4:6,3:5:7) b1(out,in0,s);
8
9 endmodule

```

```

1 //stimulus
2 module test;
3 reg in1,in0,s;
4 wire out;
5
6 mux2_to_1 m1(.in1(in1),.in0(in0),.s(s),.out(out));
7 initial
8 begin
9     in1=1'b0; in0=1'b1; s=1'b0;
10    #10 s=1'b1;
11    #10 s=1'b0;
12 end
13
14 initial
15 begin
16     $monitor($time, "in1= %b, in0= %b, s= %b, out= %b\n",in1,in0,s,out);
17 end
18
19 endmodule

```

```

0in1= 0, in0= 1, s= 0, out= x
5in1= 0, in0= 1, s= 0, out= 1
10in1= 0, in0= 1, s= 1, out= 1
14in1= 0, in0= 1, s= 1, out= x
15in1= 0, in0= 1, s= 1, out= 0
20in1= 0, in0= 1, s= 0, out= 0
23in1= 0, in0= 1, s= 0, out= x
25in1= 0, in0= 1, s= 0, out= 1

```