


WEEK 3. STRUCTURAL MODEL

1. Learn the basics of *initial* and *always* block.
2. Write testbench file for all problems in W2.pdf file.

(Problem 1, Majority, Mux 2x1, Adder circuit)

3. Encoder (8x3) and Decoder (3x8)

 - a. Construct truth table.
- b. Determine output function.
- c. Write code Verilog for that circuit: design code and simulation by testbench.



4. Flip flops (FFs): T-FF, D-FF, JK-FF, SR-FF.

- a. Draw the logic circuit of flip flops
- b. Construct truth table.
- c. Write code Verilog for those circuits: design code and simulation by testbench.

Note:

- Using structural model.
- Flip flops include reset signal.