

ET5080E

Digital Design Using Verilog HDL

Fall '21

Counters are Common
Shifters/Rotators
Parameters
Proper SM Coding
Random Misc Stuff

Administrative Matters

- Readings


- Cummings paramdesign paper for hdlcon (posted on class website)

What Have We Learned?

- 1) Sequential elements (flops & latches) should be inferred using non-blocking “`<=`” assignments
- 2) Combinational logic should be inferred using blocking “`=`” statements.
- 3) Blocking and non-Blocking statements should not be mixed in the same **always** block.
- 4) Plus 5 other guidelines of good coding outlined in the Cummings SNUG paper.

Engineers are paid to think, Pharmacists are paid to follow rules

- Counters are commonly needed blocks.

 

8-bit counter with reset & enable

Increment logic & mux are
combinational → blocking

Flop is sequential. → non-blocking

Pill Counter

```
module pill_cnt(clk,rst_n,en,cnt);

input clk,rst_n;
output [7:0] cnt;

reg [7:0] nxt_cnt,cnt;

always @(posedge clk, negedge rst_n)
  if (!rst_n)
    cnt <= 8'h00;
  else
    cnt <= nxt_cnt;

always @(en or cnt)
  if (en)
    nxt_cnt = cnt + 1; // combinational
  else
    nxt_cnt = cnt;    // so use blocking

endmodule
```

Nothing wrong with this code
Just a little verbose. Use DF?

```
module pill_cnt(clk,rst_n,en,cnt);

input clk,rst_n;
output [7:0] cnt;

reg [7:0] cnt;
wire [7:0] nxt_cnt;

always @(posedge clk, negedge rst_n)
  if (!rst_n)
    cnt <= 8'h00;
  else
    cnt <= nxt_cnt;

assign nxt_cnt (en) ? cnt+1 : cnt;

endmodule
```


I.Q. Counter (the rebel engineer)

```
module iq_cnt(clk,rst_n,en,cnt);  
input clk,rst_n;  
output [7:0] cnt;  
reg [7:0] cnt;  
always @(posedge clk or negedge rst_n)  
  if (!rst_n)  
    cnt <= 8'h00;  
  else if (en)  
    cnt <= cnt + 1; // combinational  
endmodule
```

Is this OK?

What 2 rules are broken here?

 - 1) Code infers combinational using a non-blocking assignment
- 2) We are using an if statement without a pure else clause




Ring Counter

```
module ring_counter (count, enable, clock, reset);  
  output reg    [7: 0]  count;  
  input         enable, reset, clock;  
  
  always @ (posedge clock or posedge reset)  
    if (reset == 1'b1)  count <= 8'b0000_0001;  
    else if (enable == 1'b1) begin  
      case (count)  
        8'b0000_0001: count <= 8'b0000_0010;  
        8'b0000_0010: count <= 8'b0000_0100;  
        ...  
        8'b1000_0000: count <= 8'b0000_0001;  
        default: count <= 8'bxxxx_xxxx;  
      endcase  
    end  
endmodule
```

What do you think of this code?

Ring Counter (a better way)
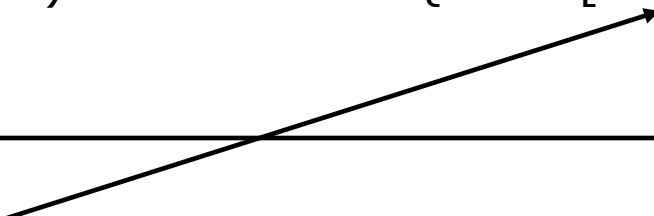
```
module ring_counter (count, enable, clock, reset_n);  
  output reg    [7: 0]  count;  
  input         enable, reset, clock;  
  
  always @ (posedge clock or negedge reset_n)  
    if (!reset_n)          count <= 8'b0000_0001;  
    else if (enable == 1'b1) count <= {count[6:0], count[7]};  
endmodule
```



- Use vector concatenation in this example to be more explicit about desired behavior/implementation
 - More concise
 - Does not rely on synthesis tool to be smart and reduce your logic for you.

Rotator

```
module rotator (Data_out, Data_in, load, clk, rst_n);  
  output reg    [7: 0]  Data_out;  
  input  [7: 0]  Data_in;  
  input          load, clk, rst_n;  
  
  always @ (posedge clk or negedge rst_n)  
    if (!rst_n)    Data_out <= 8'b0;  
    else if (load) Data_out <= Data_in;  
    else if (en)   Data_out <= {Data_out[6: 0], Data_out[7]};  
    else          Data_out <= Data_out  
endmodule
```

- Think what this code implies...How will it synthesize?
- What would such a block be used for?

Shifter

```
always @ (posedge clk) begin
  if (rst) Data_Out <= 0;
  else case (select[1:0])
    2'b00: Data_Out <= Data_Out;           // Hold
    2'b01: Data_Out <= {Data_Out[3], Data_Out[3:1]}; // ÷ by 2
    2'b10: Data_Out <= {Data_Out[2:0], 1'b0}; // X by 2
    2'b11: Data_Out <= Data_In;           // Parallel Load
  endcase
end
endmodule
```

- Think what this code implies...How will it synthesize?

- Is the reset synchronous or asynchronous?

- Why was the MSB replicated on the ÷ by 2

- There is no default to the case, is this bad?

Aside (a quick intro to parameters)

- **parameter** → like a local **define**
 - Defined locally to the module
 - Can be overridden (passed a value in an instantiation)
 - There is another method called **defparam** (don't ever use it) that can override them
- **localparam** → even more local than parameter
 - Can't be passed a value
 - **defparam** does not modify
 - Only available in Verilog 2001

Aside (a quick intro to parameters)

```
module adder(a,b,cin,sum,cout);  
  
parameter WIDTH = 8; // default is 8  
  
input [WIDTH-1:0] a,b;  
input cin;  
output [WIDTH-1:0] sum;  
output cout;  
  
assign {cout,sum} = a + b + cin  
  
endmodule
```

Instantiation of module can
override a parameter.

```
module alu(src1,src2,dst,cin,cout);  
  input [15:0] src1,src2;  
  ...  
  ///////////////////////////////////  
  // Instantiate 16-bit adder //  
  ///////////////////////////////////  
  adder #(16) add1(.a(src1),.b(src2),  
                  .cin(cin),.cout(cout),  
                  .sum(dst));  
  ...  
endmodule
```

Aside (a quick intro to parameters)

■ Examples:

```
parameter Clk2q = 1.5,  
          Tsu = 1,  
          Thd = 0;
```


```
parameter IDLE   = 2'b00;  
parameter CONV  = 2'b01;  
parameter ACCM  = 2'b10;
```

```
module register2001 #(parameter SIZE=8)  
  (output reg [SIZE-1:0] q, input [SIZE-1:0] d,  
   input clk, rst_n);  
  
  always @(posedge clk, negedge rst_n)  
    if (!rst_n) q <= 0;  
    else q <= d;  
  
endmodule
```

Verilog 2001 allows
definition in module header

- Read Cummings
paramdesign paper
for hdlcon posted on
class website

State Machines

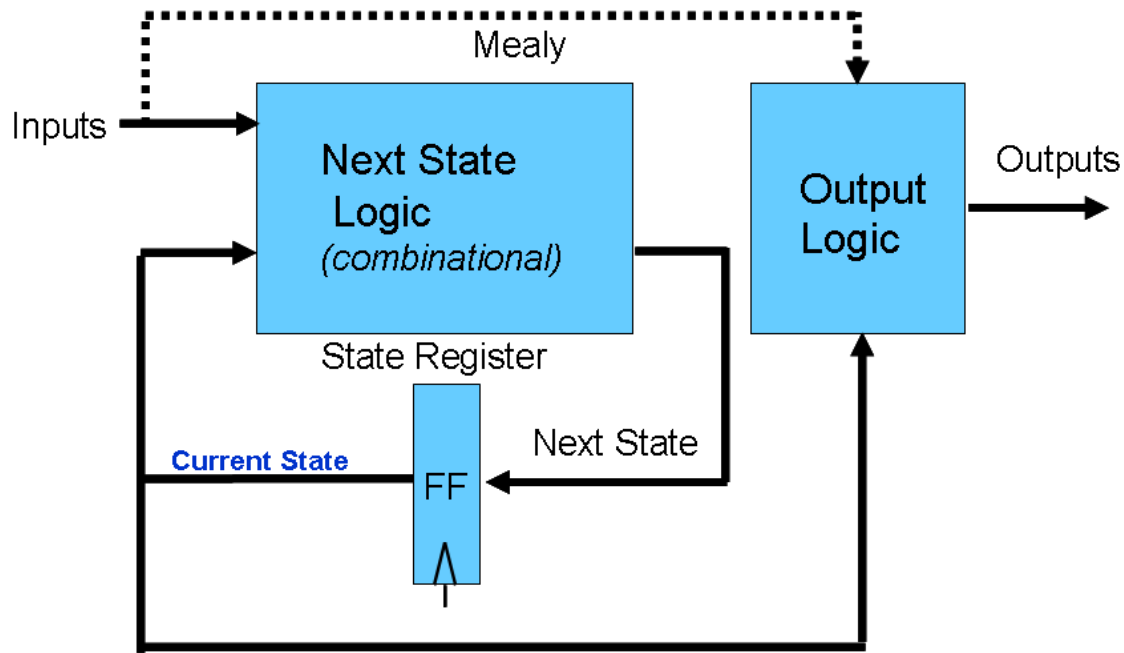


State Machines:

- Next State and output logic are combinational blocks, which have outputs dependent on the current state.
- The current state is, of course, stored by a FF.

• What is the best way to code State Machines?:

- ✓ Best to separate combinational (blocking) from sequential (non-blocking)
- ✓ Output logic and state transition logic can be coded in same **always** block since they have the same inputs
- ✓ Output logic and state transition logic are ideally suited for a **case** statement

State Diagrams

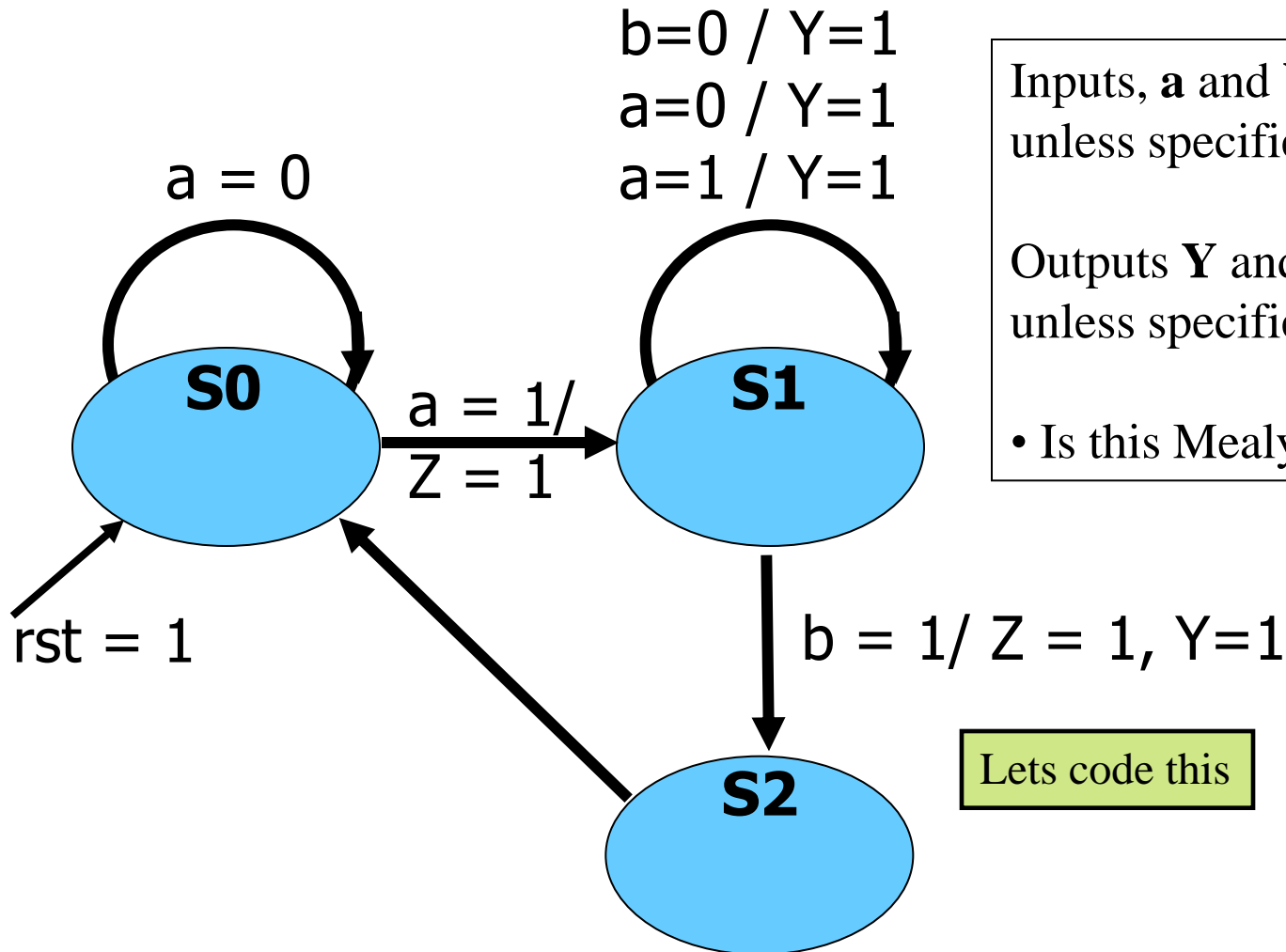

Inputs, **a** and **b** are 0, unless specified otherwise

Outputs **Y** and **Z** are 0, unless specified otherwise.

- Is this Mealy or Moore?

Lets code this

SM Coding

```
module fsm(clk,rst,a,b,Y,Z);  
  
input clk,rst,a,b;  
output Y,Z;  
  
parameter S0 = 2'b00,  
           S1 = 2'b01,  
           S2 = 2'b10;  
  
reg [1:0] state,nxt_state;  
  
always @(posedge clk, posedge rst)  
  if (rst)  
    state <= S0;  
  else  
    state <= nxt_state;
```

What problems do we have here?

```
always @ (state,a,b)  
  case (state)  
    S0 : if (a) begin  
          nxt_state = S1;  
          Z = 1; end  
      else  
          nxt_state = S0;  
    S1 : begin  
          Y=1;  
          if (b) begin  
            nxt_state = S2;  
            Z=1; end  
          else  
            nxt_state = S1;  
          end  
    S2 : nxt_state = S0;  
  endcase  
endmodule
```


SM Coding (2nd try of combinational)

```
always @ (state,a,b)
```

```
nxt_state = S0; // default to reset  
Z = 0;        // default outputs  
Y = 0;        // to avoid latches
```

```
case (state)
```

```
  S0 : if (a) begin
```

```
    nxt_state = S1;
```

```
    Z = 1;
```

```
  end
```

```
S1 : begin
```

```
  Y=1;
```

```
  if (b) begin
```

```
    nxt_state = S2;
```

```
    Z=1; end
```

```
  else nxt_state = S1;
```

```
end
```

```
default : nxt_state = S0;
```

```
endcase
```

```
endmodule
```




Defaulting of assignments and having a default to the case is highly recommended!

SM Coding Guidelines

 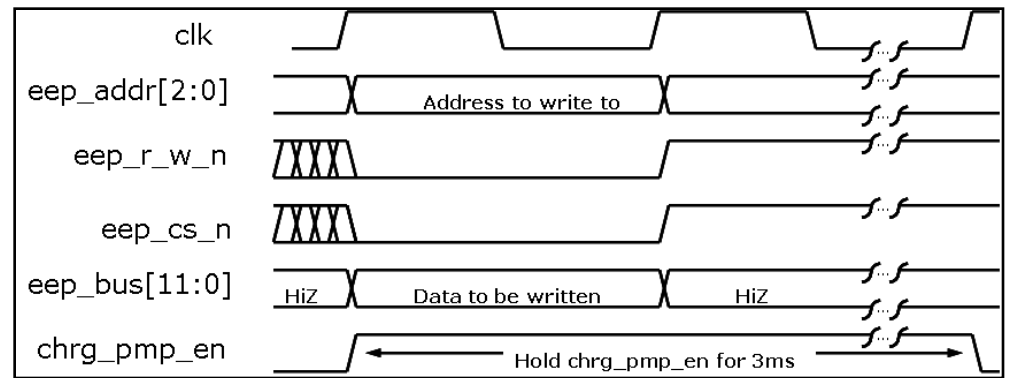 - 1) Keep state assignment in separate **always** block using non-blocking “<=“ assignment
- 2) Code state transition logic and output logic together in a **always** block using blocking assignments
- 3) Assign default values to all outputs, and the *next_state* registers. This helps avoid unintended latches
- 4) Remember to have a **default** to the **case** statement.
 - Default should be (if possible) a state that transitions to the same state as reset would take the SM to.
 - Avoids latches
 - Makes design more robust to spurious electrical/cosmic events.

SM Interacting with SM

- A very common case is a state that needs to be held for a certain time.
 - ✓ The state machine in this case may interact with a timer (counter).



Multiple levels of interaction between SM's

EEPROM Write SM Example [1]

```
module eeprom_sm(clk,por_n,wrt_eep,  
wrt_data,eep_r_w_n,eep_cs_n,  
eep_bus,chg_pmp_en,wrt_done);
```

```
parameter IDLE   = 2'b00,  
          BUS     = 2'b01,  
          CHRGE   = 2'b10;
```

```
input clk,por_n,wrt_eep;  
input [11:0] wrt_data;    // data to write  
output eep_r_w_n,eep_cs_n;  
output chg_pmp_en;       // hold for 3ms  
inout [11:0] eep_bus;
```

```
reg [13:0] tm;           // 3ms => 14-bit timer  
reg clr_tm,inc_tm,bus_wrt;  
reg [1:0] state,nxtState;
```

```
//// implement 3ms timer below ////
```

```
always @(posedge clk or  
        posedge clr_tm)  
  if (clr_tm)      tm <= 14'h0000;  
  else if (inc_tm) tm <= tm+1;
```

```
//// @4MHZ cnt of 2EE0 => 3ms ////
```

```
assign tm_eq_3ms = (tm==14'h2EE0) ?  
                  1'b1 : 1'b0;
```

```
//// implement state register below ////
```

```
always @(posedge clk or  
        negedge por_n)  
  if (!rst_n) state <= IDLE;  
  else state <= nxtState;
```


EEPROM Write SM Example [2]

```
//// state transition logic & ////  
//// output logic ////  
always @(state,wrt_eep,tm_eq_3ms)  
begin  
    nxtState = IDLE;    // default all  
    bus_wrt = 0;        // to avoid  
    clr_tm = 0;         // unintended  
    inc_tm = 0;         // latches  
    chrg_pmp_en = 0;  
  
    case (state)  
        IDLE : if (wrt_eep)  
            nxtState = BUS;  
        BUS : begin  
            clr_tm = 1;  
            bus_wrt = 1;  
            nxtState = CHRNG;  
        end
```

Are there optimizations
that can be made?

```
        default : begin        // is CHRNG  
            inc_tm = 1;  
            chrg_pmp_en=1;  
            if (tm_eq_3ms)  
                begin  
                    wrt_done = 1;  
                    nxtState = IDLE;  
                end  
            else nxtState = CHRNG;  
        end  
  
    endcase  
end  
  
    assign eep_r_w_n = ~bus_wrt;  
    assign eep_cs_n = ~bus_wrt;  
    assign eep_bus = (bus_wrt) ?  
        wrt_data : 12'bzzzz;  
  
endmodule
```

USART (RS232) Example

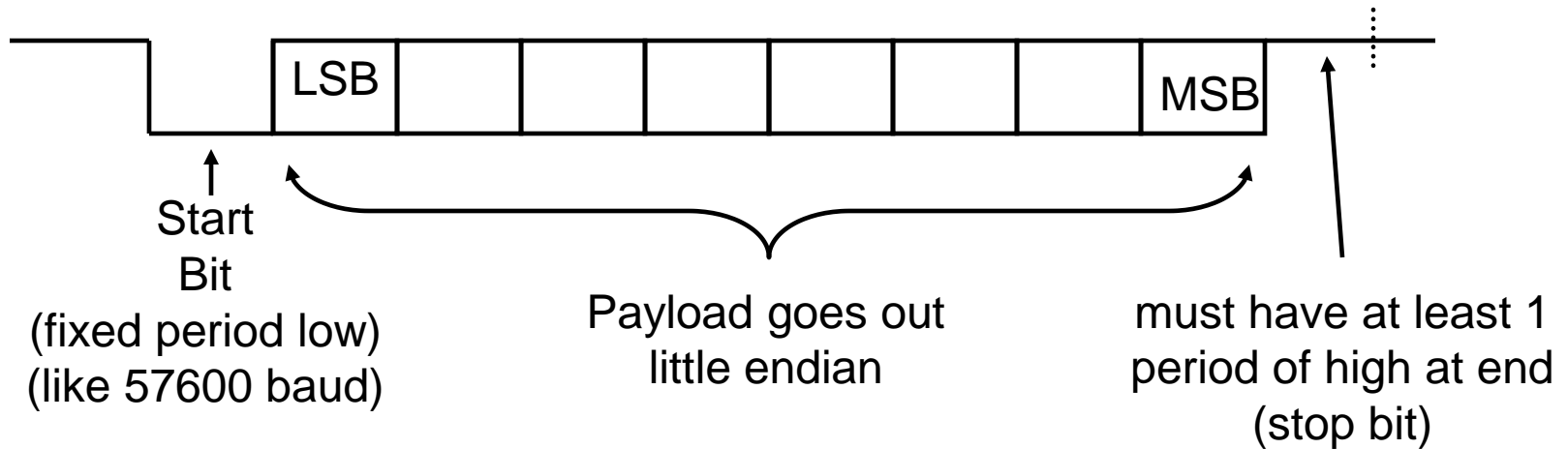

Assume we have a 4MHz clock running our digital system

We want to make a RS232 transmitter with a baud rate of 57,600

How many clock cycles do we hold each bit?

$$Cycles = \frac{4MHz}{57600baud} \approx 69$$

$$69 = 7'b1000101$$

USART Example

```
module usart_tx(clk,rst_n,strt_tx,tx_data,tx_done,TX);  
  
input clk, rst_n, strt_tx;    // start_tx comes from Master SM  
input [7:0] tx_data;          // data to transmit  
output TX;                    // TX is the serial line  
output tx_done;               // tx_done asserted back to Master SM  
    .  
    .  
    .  
endmodule;
```

- 1) Go over HW3 problem statement

Random Misc Topics

Next slides are a bunch of stuff I wasn't sure where to put, but seemed like good information.

Mux With case

```
module Mux_4_32_(output [31:0] mux_out, input [31:0] data_3,  
    data_2, data_1, data_0, input [1:0] select, input enable);  
    reg          [31: 0] mux_int;  
    // choose between the four inputs  
    always @ ( data_3 or data_2 or data_1 or data_0 or select)  
        case (select) (* synthesis parallel_case *)  
            2'b00:          mux_int = data_0;  
            2'b01:          mux_int = data_1;  
            2'b10:          mux_int = data_2;  
            2'b11:          mux_int = data_3;  
        endcase  
    // add the enable functionality  
    assign          mux_out = enable ? mux_int : 32'bz;  
endmodule
```

Synthesis directive:

Lets the synthesis tool know to use parallel (mux) scheme when synthesizing instead of priority encoding. Called an attribute in the IEEE spec

- Case statement implies priority unless use parallel_case pragma

Encoder With case

```
module encoder (output reg [2:0] Code, input [7:0] Data);  
always @ (Data)  
  // encode the data  
  case (Data)  
    8'b00000001      : Code = 3'd0;  
    8'b00000010      : Code = 3'd1;  
    8'b00000100      : Code = 3'd2;  
    8'b00001000      : Code = 3'd3;  
    8'b00010000      : Code = 3'd4;  
    8'b00100000      : Code = 3'd5;  
    8'b01000000      : Code = 3'd6;  
    8'b10000000      : Code = 3'd7;  
    default          : Code = 3'bxxx; // invalid, so don't care  
  endcase  
endmodule
```


How do we think it will
synthesize?

Priority Encoder With **case**

```
module priority_encoder (output reg [2:0] Code, output valid_data,  
    input [7:0] Data);  
  
assign valid_data = |Data; // "reduction or" operator  
always @ (Data)  
    // encode the data  
    case (Data)  
        8'b1xxxxxxx : Code = 7;  
        8'b01xxxxxx : Code = 6;  
        8'b001xxxxx : Code = 5;  
        8'b0001xxxx : Code = 4;  
        8'b00001xxx : Code = 3;  
        8'b000001xx : Code = 2;  
        8'b0000001x : Code = 1;  
        8'b00000001 : Code = 0;  
        default      : Code = 3'bxxx; // should be at least one 1, don't care  
    endcase  
endmodule
```

Seven Segment Display

```
module Seven_Seg_Display (Display, BCD, Blanking);  
  output reg [6: 0]      Display;           // abc_defg  
  input [3: 0]          BCD;  
  input                  Blanking;  
  
  parameter    BLANK    = 7'b111_1111;      // active low  
  parameter    ZERO     = 7'b000_0001;      // h01  
  parameter    ONE      = 7'b100_1111;      // h4f  
  parameter    TWO      = 7'b001_0010;      // h12  
  parameter    THREE    = 7'b000_0110;      // h06  
  parameter    FOUR     = 7'b100_1100;      // h4c  
  parameter    FIVE     = 7'b010_0100;      // h24  
  parameter    SIX      = 7'b010_0000;      // h20  
  parameter    SEVEN    = 7'b000_1111;      // h0f  
  parameter    EIGHT    = 7'b000_0000;      // h00  
  parameter    NINE     = 7'b000_0100;      // h04
```

 

Defined constants – can make code more understandable!

Seven Segment Display [2]

```
always @ (BCD or Blanking)
  if (Blanking) Display = BLANK;
  else
    case (BCD)
      4'd0:      Display = ZERO;
      4'd1:      Display = ONE;
      4'd2:      Display = TWO;
      4'd3:      Display = THREE;
      4'd4:      Display = FOUR;
      4'd5:      Display = FIVE;
      4'd6:      Display = SIX;
      4'd7:      Display = SEVEN;
      4'd8:      Display = EIGHT;
      4'd9:      Display = NINE;
      default:   Display = BLANK;
    endcase
  endmodule
```

***Using the
defined
constants!***

Inter vs Intra Statement Delays

- Inter-assignment delays block both evaluation and assignment
 - #4 c = d;
 - #8 e = f;
- Intra-assignment delays block assignment but not evaluation
 - c = #4 d;
 - e = #8 f;
- Blocking statement is still blocking though, so evaluation of next statements RHS still does not occur until after the assignment of the previous expression LHS.
 - What?? How is it any different then? Your confusing me!

Inter vs Intra Statement Delays (Blocking Statements)

```
module inter();  
integer a,b;  
  
initial begin  
    a=3;  
  
    #6 b = a + a;  
    #4 a = b + a;  
  
end  
endmodule
```

Compare these two
modules

```
module intra();  
integer a,b;  
  
initial begin  
    a=3;  
  
    b = #6 a + a;  
    a = #4 b + a;  
  
end  
endmodule
```

Time	Event
0	a=3
6	b=6
10	a=9

Yaa, Like I said, they
are the same!

Or are they?

Time	Event
0	a=3
6	b=6
10	a=9

Intra Statement Delays (Blocking Statements)

```
module inter2();  
integer a,b;
```

```
initial begin
```

```
  a=3;
```

```
  #6 b = a + a;
```

```
  #4 a = b + a;
```

```
end
```

```
initial begin
```

```
  #3 a=1;
```

```
  #5 b=3;
```

```
end
```

```
endmodule
```

Time	Event
0	a=3
3	a=1
6	b=2
8	b=3
10	a=4

```
module inter2();  
integer a,b;
```

```
initial begin
```

```
  a=3;
```

```
  b = #6 a + a;
```

```
  a = #4 b + a;
```

```
end
```

```
initial begin
```

```
  #3 a=1;
```

```
  #5 b=3;
```

```
end
```

```
endmodule
```

Time	Eval Event	Assign Event
0	nxt_b= 6	a=3
3	--	a=1
6	nxt_a=7	b=6
8	--	b=3
10	--	a=7

Non-Blocking: Inter-Assignment Delay

- Delays both the evaluation and the update

```
always @(posedge clk) begin  
    b <= a + a;  
    # 5 c <= b + a;  
    # 2 d <= c + a;  
end  
  
initial begin  
    a = 3; b = 2; c = 1;  
end
```

Time	Event
0	clk pos edge
0	b=6
5	c=9
7	c=12

Non-Blocking: Inter-Assignment Delay

- Delays both the evaluation and the update

```
always @(posedge clk) begin  
    b <= a + a;  
    c <= #5 b + a;  
    d <= #2 c + a;  
end  
  
initial begin  
    a = 3; b = 2; c = 1;  
end
```

Time	Event
0	clk pos edge
0	b=6
2	d=4
5	c=5

This is more like modeling the Clk2Q delay of a Flop
(it captures on rising edge, but has a delay till output)

Intra-Assignment Review

```
module bnb;  
reg a, b, c, d, e, f;
```

```
initial begin // blocking assignments  
    a = #10 1; // a will be assigned 1 at time 10  
    b = #2 0; // b will be assigned 0 at time 12  
    c = #4 1; // c will be assigned 1 at time 16  
end
```

```
initial begin // non-blocking assignments  
    d <= #10 1; // d will be assigned 1 at time 10  
    e <= #2 0; // e will be assigned 0 at time 2  
    f <= #4 1; // f will be assigned 1 at time 4  
end  
endmodule
```

Note: In testbenches I mainly find blocking inter-assignment delays to be the most useful. Delays really not used outside of testbenches that much during the design process.