

Chapter 9

Chapter 9. Useful Modelling Techniques

9.7 Exercises

1. Using assign and deassign statements, design a positive edge-triggered D-flipflop with asynchronous clear (q=0) and preset (q=1).


My answer:

```
1 //ex9-1 a possitive edge-triggered D_flipflop with asynchronous clear and preet.
2
3 module edge_dff(q,qbar,d,clk,reset);
4
5 //I/O prots
6 output reg q,qbar;
7 input d,clk,reset;
8
9 always @(posedge clk)
10 begin
11     q=d;
12     qbar=~d;
13 end
14
15 always @(reset)
16     if(reset)
17     begin
18         assign q=1'b0;
19         assign qbar=1'b1;
20     end
21     else
22     begin
23         deassign q;
24         deassign qbar;
25     end
26
27 endmodule
```

```

1  module test;
2
3  reg d,clk,reset;
4  wire q,qbar;
5
6  edge_dff d1(q,qbar,d,clk,reset);
7
8  initial
9  begin
10     d=1'b1;
11     reset=1'b0;
12     #34 reset=1'b1;
13     #60 reset=1'b0;
14     #150 reset=1'b1;
15 end
16
17 initial
18 begin
19     clk=1'b0;
20     forever #10 clk=~clk;
21 end
22
23 endmodule

```

 

2. Using primitive gates, design a 1-bit full adder FA. Instantiate the full adder inside a stimulus module. Force the sum output to a & b & c_in for the time between 15 and 35 units.

My answer:

```
1 //ex9_2 a 1-bit full adder
2
3 module fa(a,b,cin,cout,sum);
4     output sum,cout;
5     input a,b,cin;
6
7     wire c1,c2,c3,s1,s2,s3,s4;
8
9     and a1(c1,b,cin),
10        a2(c2,a,b),
11        a3(c3,a,cin);
12
13     or o1(cout,c1,c2,c3); //generate cout
14
15     and a4(s1,~a,~b,cin),
16        a5(s2,~a,b,~cin),
17        a6(s3,a,b,cin),
18        a7(s4,a,~b,~cin);
19
20     or o2(sum,s1,s2,s3,s4); //generate sum
21
22 endmodule
```

```

1 //stimulus
2
3 module test;
4
5 reg a,b,cin;
6 wire cout,sum;
7
8 fa f1(a,b,cin,cout,sum);
9
10 initial
11 begin
12 a=1'b0;
13 b=1'b1;
14 cin=1'b0;
15 #50 cin=1'b1;
16 end
17
18 initial
19 begin
20 #15 force sum=a&b&cin;
21 #20 release sum;
22 end
23
24 initial
25 $monitor($time , " sum= %b",sum);
26
27 endmodule

```

```

0 sum= 1
15 sum= 0
35 sum= 1
50 sum= 0

```

3. A 1-bit full adder FA is defined with gates and with delay parameters as shown below.

// Define a 1-bit full adder

module fulladd(sum,c_out,a,b,c_in);

parameter d_sum=0,d_cout=0;

//I/O port declarations

output sum,c_out;

input a,b,c_in;

//Internal nets

```

wire s1,c1,c2;

//Instantiate logic gate primitives
xor(s1,a,b);
and(c1,a,b);
xor #(d_sum) (sum,s1,c_in); //delay on output sum is d_sum
and (c2,s1,c_in);
or #(d_out) (c_out,c2,c1); //delay on output c_out is d_cout
endmodule

```

Define a 4-bit full adder fulladd4 as shown in example 5-8, but pass the following parameter values to the instances, using the two methods discussed in the book.

Instance	Delay Values
fa0	d_sum=1,d_cout=1
fa1	d_sum=2,d_cout=2
fa2	d_sum=2,d_cout=2
fa3	d_sum=3,d_cout=3

a. Build the fulladd4 module with defparm statements to change instance parameter values. Simulate the 4-bit full adder using the stimulus shown in example 5-9 . Explain the effect of the full adder delays on the times when outputs of the adder appear. (Use delays of 20 instead of 5 used in this stimulus.)

b. Build the fulladd4 with delay values passed to instances fa0, fa1, fa2, fa3 during instantiation. Resimulate the 4-bit adder, using the stimulus above. Check if the results are identical.

My answer:

```
1 // 4-bit full adder
2 module fulladd4(sum,c_out,a,b,c_in);
3
4     output [3:0] sum;
5     output c_out;
6     input [3:0] a,b;
7     input c_in;
8
9     wire c1,c2,c3;
10
11     defparam fa0.d_sum=1,fa0.d_cout=1,
12             fa1.d_sum=2,fa1.d_cout=2,
13             fa2.d_sum=3,fa2.d_cout=3,
14             fa3.d_sum=4,fa3.d_cout=4;
15
16     fulladd fa0 (sum[0],c1,a[0],b[0],c_in);
17     fulladd fa1 (sum[1],c2,a[1],b[1],c1);
18     fulladd fa2 (sum[2],c3,a[2],b[2],c2);
19     fulladd fa3 (sum[3],c_out,a[3],b[3],c3);
20
21 endmodule
```



```

1 //stimulus
2 module stimulus;
3
4 reg [3:0] A,B;
5 reg C_IN;
6 wire [3:0] SUM;
7 wire C_OUT;
8
9 fulladd4 f1(SUM,C_OUT,A,B,C_IN);
10
11 initial
12 begin
13     $monitor($time, " A= %b, B=%b, C_IN=%b,--- C_OUT=%b, SUM= %b\n",
14             A,B,C_IN,C_OUT,SUM);
15 end
16
17 initial
18 begin
19     A=4'd0; B=4'd0; C_IN=1'b0;
20     #20 A=4'd3; B=4'd4;
21     #20 A=4'd2; B=4'd5;
22     #20 A=4'd9; B=4'd9;
23     #20 A=4'd10; B=4'd15;
24     #20 A=4'd10; B=4'd5; C_IN=1'b1;
25 end
26
27 endmodule

```

```

0 A= 0000, B=0000, C_IN=0,--- C_OUT=x, SUM= xxxx
1 A= 0000, B=0000, C_IN=0,--- C_OUT=x, SUM= xxx0
3 A= 0000, B=0000, C_IN=0,--- C_OUT=x, SUM= xx00
4 A= 0000, B=0000, C_IN=0,--- C_OUT=0, SUM= xx00
5 A= 0000, B=0000, C_IN=0,--- C_OUT=0, SUM= x000
7 A= 0000, B=0000, C_IN=0,--- C_OUT=0, SUM= 0000
20 A= 0011, B=0100, C_IN=0,--- C_OUT=0, SUM= 0000
21 A= 0011, B=0100, C_IN=0,--- C_OUT=0, SUM= 0001
22 A= 0011, B=0100, C_IN=0,--- C_OUT=0, SUM= 0011
23 A= 0011, B=0100, C_IN=0,--- C_OUT=0, SUM= 0111
40 A= 0010, B=0101, C_IN=0,--- C_OUT=0, SUM= 0111
60 A= 1001, B=1001, C_IN=0,--- C_OUT=0, SUM= 0111
61 A= 1001, B=1001, C_IN=0,--- C_OUT=0, SUM= 0110
63 A= 1001, B=1001, C_IN=0,--- C_OUT=0, SUM= 0010
64 A= 1001, B=1001, C_IN=0,--- C_OUT=1, SUM= 0010
80 A= 1010, B=1111, C_IN=0,--- C_OUT=1, SUM= 0010
81 A= 1010, B=1111, C_IN=0,--- C_OUT=1, SUM= 0011
83 A= 1010, B=1111, C_IN=0,--- C_OUT=1, SUM= 0001
89 A= 1010, B=1111, C_IN=0,--- C_OUT=1, SUM= 1001
100 A= 1010, B=0101, C_IN=1,--- C_OUT=1, SUM= 1001
101 A= 1010, B=0101, C_IN=1,--- C_OUT=1, SUM= 1000
104 A= 1010, B=0101, C_IN=1,--- C_OUT=1, SUM= 0000

```

```

1 // 4-bit full adder
2 module fulladd4(sum,c_out,a,b,c_in);
3
4     output [3:0] sum;
5     output c_out;
6     input [3:0] a,b;
7     input c_in;
8
9     wire c1,c2,c3;
10
11     /*defparam fa0.d_sum=1,fa0.d_cout=1,
12         fa1.d_sum=2,fa1.d_cout=2,
13         fa2.d_sum=3,fa2.d_cout=3,
14         fa3.d_sum=4,fa3.d_cout=4;*/
15
16     fulladd #(.d_sum(1),.d_cout(1)) fa0(sum[0],c1,a[0],b[0],c_in);
17     fulladd #(.d_sum(2),.d_cout(2)) fa1(sum[1],c2,a[1],b[1],c1);
18     fulladd #(.d_sum(3),.d_cout(3)) fa2(sum[2],c3,a[2],b[2],c2);
19     fulladd #(.d_sum(4),.d_cout(4)) fa3(sum[3],c_out,a[3],b[3],c3);
20
21 endmodule

```

```

0 A= 0000, B=0000, C_IN=0,--- C_OUT=x, SUM= xxxx
1 A= 0000, B=0000, C_IN=0,--- C_OUT=x, SUM= xxx0
3 A= 0000, B=0000, C_IN=0,--- C_OUT=x, SUM= xx00
4 A= 0000, B=0000, C_IN=0,--- C_OUT=0, SUM= xx00
5 A= 0000, B=0000, C_IN=0,--- C_OUT=0, SUM= x000
7 A= 0000, B=0000, C_IN=0,--- C_OUT=0, SUM= 0000
20 A= 0011, B=0100, C_IN=0,--- C_OUT=0, SUM= 0000
21 A= 0011, B=0100, C_IN=0,--- C_OUT=0, SUM= 0001
22 A= 0011, B=0100, C_IN=0,--- C_OUT=0, SUM= 0011
23 A= 0011, B=0100, C_IN=0,--- C_OUT=0, SUM= 0111
40 A= 0010, B=0101, C_IN=0,--- C_OUT=0, SUM= 0111
60 A= 1001, B=1001, C_IN=0,--- C_OUT=0, SUM= 0111
61 A= 1001, B=1001, C_IN=0,--- C_OUT=0, SUM= 0110
63 A= 1001, B=1001, C_IN=0,--- C_OUT=0, SUM= 0010
64 A= 1001, B=1001, C_IN=0,--- C_OUT=1, SUM= 0010
80 A= 1010, B=1111, C_IN=0,--- C_OUT=1, SUM= 0010
81 A= 1010, B=1111, C_IN=0,--- C_OUT=1, SUM= 0011
83 A= 1010, B=1111, C_IN=0,--- C_OUT=1, SUM= 0001
89 A= 1010, B=1111, C_IN=0,--- C_OUT=1, SUM= 1001
100 A= 1010, B=0101, C_IN=1,--- C_OUT=1, SUM= 1001
101 A= 1010, B=0101, C_IN=1,--- C_OUT=1, SUM= 1000
104 A= 1010, B=0101, C_IN=1,--- C_OUT=1, SUM= 0000

```


4. Create a design that uses the full adder example above. Use a conditional compilation (``ifdef`). compile the fulladd4 with defparam statements if the text macro DPARAM is defined by the ``define` statement; otherwise, compile the fulladd4 with module instance parameter values.

My answer:

```
1      //ex9-4 ifdef
2
3      `ifdef DPARAM
4      module fulladd4_d;
5          ...
6      endmodule
7      `else
8      module fulladd4_p;
9          ...
10     endmodule
11     `endif
```

6. What will be the output of the `$display` statement shown below?

```
1      //Ex9-6
2
3      module top;
4          A a1();
5      endmodule
6
7      module A;
8          B b1();
9      endmodule
10
11     module B;
12         initial
13             $display("I am inside instance %m");
14     endmodule
```

My answer:

I am inside instance top.a1.b1

7. Consider the 4-bit full adder in example 6-4. Write a stimulus file to do random testing of the full adder. Use a random number generator to generate a 32-bit random number. Pick bit 3:0 and apply them to input a; pick bits 7:4 and apply them to input b. Use bit 8 and apply it to c_in. Apply 20 random test vectors and observe the output

My answer:

```
1 //stimulus
2
3 module test;
4
5 reg [3:0] a,b;
6 reg c_in;
7 wire c_out;
8 wire [3:0] sum;
9
10 reg [31:0] addr;
11
12 fulladd4 f1(sum,c_out,a,b,c_in);
13
14 initial
15 begin
16
17     repeat (20)
18     begin
19         #10 addr=$random;
20         a=addr[3:0];
21         b=addr[7:4];
22         c_in=addr[8];
23     end
24 end
25
26 initial
27     $monitor($time, " a= %b, b= %b, c_in= %b, c_out= %b, sum= %b",
28             a,b,c_in,c_out,sum);
29
30 endmodule
```

```

0 a= xxxx, b= xxxx, c_in= x, c_out= x, sum= xxxx
10 a= 0100, b= 0010, c_in= 1, c_out= 0, sum= 0111
20 a= 0001, b= 1000, c_in= 0, c_out= 0, sum= 1001
30 a= 1001, b= 0000, c_in= 0, c_out= 0, sum= 1001
40 a= 0011, b= 0110, c_in= 0, c_out= 0, sum= 1001
50 a= 1101, b= 0000, c_in= 1, c_out= 0, sum= 1110
60 a= 1101, b= 1000, c_in= 1, c_out= 1, sum= 0110
70 a= 0101, b= 0110, c_in= 0, c_out= 0, sum= 1011
80 a= 0010, b= 0001, c_in= 0, c_out= 0, sum= 0011
90 a= 0001, b= 0000, c_in= 1, c_out= 0, sum= 0010
100 a= 1101, b= 0000, c_in= 1, c_out= 0, sum= 1110
110 a= 0110, b= 0111, c_in= 1, c_out= 0, sum= 1110
120 a= 1101, b= 0011, c_in= 1, c_out= 1, sum= 0001
130 a= 1101, b= 1110, c_in= 1, c_out= 1, sum= 1100
140 a= 1100, b= 1000, c_in= 1, c_out= 1, sum= 0101
150 a= 1001, b= 1111, c_in= 1, c_out= 1, sum= 1001
160 a= 0110, b= 1100, c_in= 0, c_out= 1, sum= 0010
170 a= 0101, b= 1100, c_in= 0, c_out= 1, sum= 0001
180 a= 1010, b= 1010, c_in= 0, c_out= 1, sum= 0100
190 a= 0101, b= 1110, c_in= 1, c_out= 1, sum= 0100
200 a= 0111, b= 0111, c_in= 0, c_out= 0, sum= 1110

```

8. Use the 8-bit memory initialization example in example 9-14 . Modify the file to read data in hexadecimal. Write a new data file with the following addresses and data values. Unspecified locations are not initialized.

Location Address	Data
1	33
2	66
4	z0
5	0z
6	01

My answer:

```
1 //ex9-8
2 module test;
3
4 reg [7:0] memory [0:7];
5 integer i;
6
7 initial
8 begin
9     $readmemh("init.dat",memory);
10
11     for(i=0;i<8;i=i+1)
12         $display("Memory [%0d] = %h",i,memory[i]);
13 end
14
15 endmodule
```

```
# Memory [0] = xx
# Memory [1] = 33
# Memory [2] = 66
# Memory [3] = xx
# Memory [4] = z0
# Memory [5] = 0z
# Memory [6] = 01
# Memory [7] = xx
```

9. Write an initial block that controls the VCD file. The initial block must do the following:

I Set myfile.dmp as the output VCD file.

I Dump all variables two levels deep in module instance top.a1.b1.c1.

I Stop dumping to VCD at time 200.

I Start dumping to VCD at time 400.

I Stop dumping to VCD at time 500.

I Create a checkpoint. Dump the current value of all VCD variables to the dumpfile.

My answer:

```
1 //ex9-9
2
3 initial
4     $dumpfile("myfile.dump");
5
6 initial
7     $dumpvars(2,top.a1.b1.c1);
8
9 initial
10 begin
11     #200 $dumpoff;
12     #200 $dumpon;
13     #100 $dumpoff;
14 end
15
16 initial
17     $dumpall;
```