

ET5080E

Digital Design Using Verilog HDL

Fall '21

Lecture 2

- Verilog Syntax
- Structural Verilog
- Timing in Verilog

Administrative Matters

■ Readings

- Chapter 4 (module and port declaration, hierarchical naming...and you thought chapter 3 was boring?)
- Chapter 5 (structural, gate primitives, delays)

Comments in Verilog

- Commenting is important
 - In industry many other poor schmucks are going to read your code
 - Some poor schmuck (perhaps you 4 years later) are going to have to reference your code when a customer discovers a bug.
- The best comments document why you are doing what you are doing, not what you are doing.
 - Any moron who knows verilog can tell what the code is doing.
 - Comment why (motivation/thought process) you are doing that thing.

Commenting in Verilog

```
always @(posedge clk)

begin
    Sig_FF1 <= Sig           // Capture value of Sig Line in FF
    Sig_FF2 <= Sig_FF1;      // Flop Sig_FF1 to form Sig_FF2
    Sig_FF3 <= Sig_FF2;      // Flow Sig_FF2 to form Sig_FF3
end

// start_bit is ~Sig_FF2 & Sig_FF3
assign start_bit = (~Sig_FF2 && Sig_FF3) ? 1'b1 : 1'b0;
```

(Read with sarcasm)

“Thanks for the commenting the code pal. It tells me so much more than the verilog itself”.

Commenting in Verilog

```
always @(posedge clk)
/******
 * Sig is asynchronous and has to be double flopped *
 * for meta-stability reasons prior to use *****/
*****/
begin
    Sig_FF1 <= Sig;
    Sig_FF2 <= Sig_FF1; // double flopped meta-stability free
    Sig_FF3 <= Sig_FF2; // flop again for use in edge detection
end

/******
 * Start bit in protocol initiated by falling edge of Sig line *
 *****/
assign start_bit = (~Sig_FF2 && Sig_FF3) ? 1'b1 : 1'b0;
```

Can see 2 types
of comments.

Comment to
end of line is //

Multi line
comment starts
with /* and
ends with */

- This is better commenting. It tells you why stuff was done

Numbers in Verilog

- General format is: `<size>'<base><number>`
- Examples:
 - `4'b1101` // this is a 4-bit binary number equal to 13
 - `10'h2e7` // this is a 10-bit wide number specified in hex
- Available bases:
 - d = decimal (please only use in test benches)
 - h = hex (use this frequently)
 - b = binary (use this frequently for smaller #'s)
 - o = octal (who thinks in octal?, please avoid)

Numbers in Verilog

- Numbers can have x or z characters as values
 - x = unknown, z = High Impedance
 - 12'h13x // 12-bit number with lower 4-bits unknown

- If size is not specified then it depends on simulator/machine.
 - Always size the number for the DUT verilog
 - ✓ Why create 32-bit register if you only need 5 bits?
 - ✓ May cause compilation errors on some compilers

- Supports negative numbers as well
 - -16'h3A // this would be -3A in hex (i.e. FFC6 in 2's complement)
 - I rarely if ever use this. I prefer to work 2's complement directly

Identifiers (Signal Names)



- Identifiers are the names you choose for your signals
- In a programming language you should choose descriptive variable names. In a HDL you should choose descriptive signal names.
 - Use mixed case and/or `_` to delimit descriptive names.
 - ✓ `assign parityErr = ^serial_reg;`
 - ✓ `nxtState = returnRegister;`
 - Have a convention for signals that are active low
 - ✓ Many errors occur on the interface between blocks written by 2 different people. One assumed a signal was active low, and the other assumed it was active high
 - ✓ I use `_n` at the end of a signal to indicate active low
 - ✓ `rst_n = 1'b0` `// assert reset`

Signal Values & Strength in Verilog

- Signals can have 1 of 4 values

Need high impedance for modeling of tri-state busses


Value:	Meaning:
0	Logic zero, false condition
1	Logic one, true condition
x	Unknown, either uninitialized or in contention
z	High impedance. Not driven, or not connected

  


What value does q have prior to any positive clock edge?

It is unknown: **x** (uninitialized)


Resolving 4-Value Logic

 


A	B	OUT
0	0	0
0	1	1
1	1	1
0	x	x
0	z	x
1	x	1
1	z	1

 

A	B	OUT
0	0	0
0	1	0
1	1	1
0	x	0
0	z	0
1	x	x
1	z	x

 

S	A	T	B	OUT
0	0	z	z	z
0	1	z	x	x
0	x	z	1	1
0	z	z	0	0
1	0	0	1	x
1	0	0	z	0
1	1	1	z	1
1	x	x	z	x
1	z	x	0	x

 


A	0	1	x	z
OUT	1	0	x	x

Signal Values & Strength in Verilog

Strength Level	Meaning:
supply	Strongest (like a supply VDD or VSS)
strong	Strong (default if not specified)
pull	Medium strength (like a pullup device)
weak	Weak, like a keeper (sustainer, leaker)
highz	High impedance

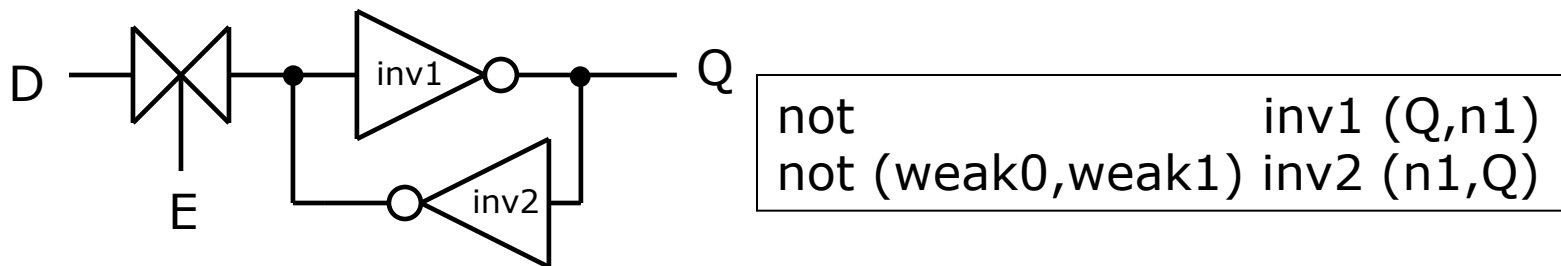- Concept of drive strength supported to model certain CMOS circuits that utilize contention.



Registers in Verilog

- Registers are storage nodes
 - They retain their value till a new value is assigned
 - Unlike a net (wire) they do not need a driver
 - Can be changed in simulation by assigning a new value

- Registers are not necessarily FlipFlops
 - In your DUT Verilog registers are typically FlipFlops
 - Anything assigned in an *always* or *initial* block must be assigned to a register
 - You will use registers in your testbenches, but they will not be FlipFlops

Vectors in Verilog

- Vectors are a collection of bits (i.e. 16-bit wide bus)

```
////////////////////////////////////  
// Define the 16-bit busses going in and out of the ALU //  
////////////////////////////////////  
wire [15:0] src1_bus,src2_bus,dst_bus;
```

```
////////////////////////////////////  
// State machine has 8 states, need a 3-bit encoding //  
////////////////////////////////////  
reg [2:0] state,nxt_state;
```


- Bus \neq Vector (how are they different?)

Vectors in Verilog

- Can select parts of a vector (single bit or a range)

```
module lft_shift(src,shft_in,result,shft_out);
```
 
```
input [15:0] src;  
input shft_in;  
output [15:0] result;  
output shft_out;
```



```
////////////////////////////////////  
// Can access 15 LSB's of src with [14:0] selector //  
// { , } is a process of concatenating two vectors to form one //  
////////////////////////////////////  
assign result = {src[14:0],shft_in};
```


```
assign shft_out = src[15]; // can access a single bit MSB with [15]
```

```
endmodule
```

Arrays & Memories

- Can have multi-dimensional arrays
 - `reg [7:0] mem[0:99][0:3]; // what is this?`
- Often have to model memories
 - RF, SRAM, ROM, Flash, Cache
 - Memories can be useful in your test bench
 
```
wire [15:0] src1,src2;           // source busses to ALU
reg [15:0] reg_file[0:31];      // Register file of 32 16-bit words
reg [4:0] addr1,addr2;          // src1 and src2 address
.
.
.
src1 = reg_file[addr1];          // transfer addressed register file
                                // to src1 bus
```



Parameters & Define

- Parameters are useful to make your code more generic/flexible. Read about it in text. More later...
- ``define` statement can make code more readable

```
`define idle = 2'b00; // idle state of state machine
`define conv = 2'b01; // in this state while A2 is 1
`define avg = 2'b10; // in this state while A2 is 0 and 2 samples
:
:
case (state)
  `idle : if (start_conv) state = `conv;
         else state = `idle
  `conv : if (A2) state = `avg;
         else state = `conv;
```

Bad Example... Don't Use ``define` for state assignment
Use parameters instead. ``define` should be truly global thing

Parameters & Define

```
localparam idle =          2'b00;  // idle state of state machine
localparam conv =          2'b01;  // in this state while A2D converting
localparam accum =         2'b10;  // in this state while averaging samples
.
.
.
case (state)
  idle : if (start_conv) nxt_state = conv;
        else                nxt_state = idle

  conv : if (gt) nxt_state = avg;
        else    nxt_state = conv;
.
.
.
```

- Read Cumming's paper on use of define & param. Posted on web under "supplemental"

Useful System Tasks

- `$display` → Like `printf` in C. Useful for testbenches and debug

```
$display("At time %t count = %h",$time,cnt);
```

- `$stop` → Stops simulation and allows you to still probe signals and debug
- `$finish` → completely stops simulation, simulator relinquishes control of thread.
- Also useful is ``include` for including code from another file (like a header file)
- Read about these features of verilog in your text

Full Adder: Structural

```
module half_add (X, Y, S, C);  
  
input X, Y ;  
output S, C ;  
  
xor SUM (S, X, Y);  
and CARRY (C, X, Y);  
  
endmodule
```

```
module full_add (A, B, CI, S, CO) ;  
  
input A, B, CI ;  
output S, CO ;  
  
wire S1, C1, C2;  
  
// build full adder from 2 half-adders  
half_add PARTSUM (A, B, S1, C1),  
                SUM (S1, CI, S, C2);  
  
// ... add an OR gate for the carry  
or CARRY (CO, C2, C1);  
  
endmodule
```

Full Adder: RTL/Dataflow

```
module fa_rtl (A, B, CI, S, CO) ;  
  
input A, B, CI ;  
output S, CO ;  
  
// use continuous assignments  
assign S = A ^ B ^ CI;  
assign CO = (A & B) | (A & CI) | (B & CI);  
  
endmodule
```

Data flow Verilog is
often very concise
and still easy to read

Works great for most
boolean and even
datapath descriptions

Full Adder: Behavioral

- Circuit “reacts” to given events (for simulation)
 - Actually list of signal changes that affect output

```
module fa_bhv (A, B, CI, S, CO) ;  
  
input A, B, CI;  
output S, CO;  
reg S, CO;           // assignment made in an always block  
                     // must be made to registers  
  
// use procedural assignments  
always@(A or B or CI)  
begin  
    S = A ^ B ^ CI;  
    CO = (A & B) | (A & CI) | (B & CI);  
end  
endmodule
```

Full Adder: Behavioral


■ IN SIMULATION

- When **A**, **B**, or **C** change, **S** and **CO** are recalculated

■ IN REALITY

- Combinational logic – no “waiting” for the trigger
- Constantly computing - think transistors and gates!
- Same hardware created for all three types of verilog

```
always@(A or B or CI)
begin
    S = A ^ B ^ CI;
    CO = (A & B) | (A & CI) | (B & CI);
end
```

 

Structural Basics: Primitives

- Build design up from the gate/flip-flop/latch level
 - Structural verilog is a netlist of blocks and connectivity
- Verilog provides a set of gate primitives
 - and, nand, or, nor, xor, xnor, not, buf, bufif1, etc.
 - Combinational building blocks for structural design
 - Known “behavior”
 - Cannot access “inside” description
- Can also model at the transistor level
 - Most people don’t, we won’t

Primitives

- No declarations - can only be instantiated
- Output port appears before input ports
- Optionally specify: instance name and/or delay (discuss delay later)

and N25 (Z, A, B, C); // name specified

and #10 (Z, A, B, X),

 (X, C, D, E); // delay specified, 2 gates

and #10 N30 (Z, A, B); // name and delay specified

Syntax For Structural Verilog

- First declare the interface to the module
 - Module keyword, module name
 - Port names/types/sizes
- Next, declare any internal wires using “wire”
 - wire [3:0] partialsum;
- Then instantiate the primitives/submodules
 - Indicate which signal is on which port
- ModelSim Example with ring oscillator


Hierarchy

- Any Verilog design you do will be a module
- This includes testbenches!


- Interface (“black box” representation)
 - Module name, ports
- Definition
 - Describe functionality of the block
- Instantiation
 - Use the module inside another module

Hierarchy

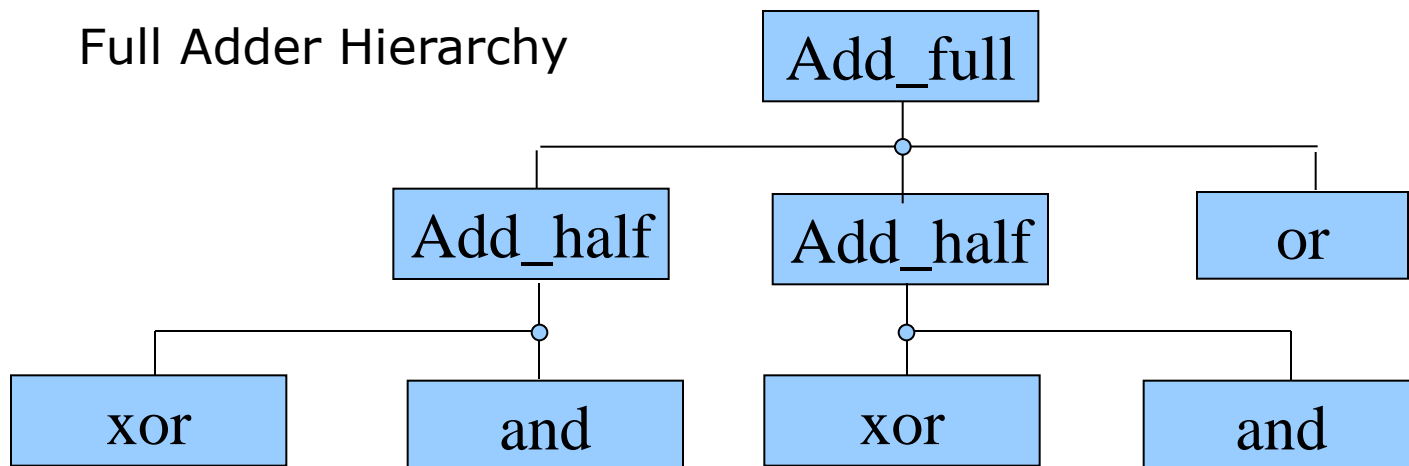- Build up a module from smaller pieces
 - Primitives
 - Other modules (which may contain other modules)
- Design: typically top-down
- Verification: typically bottom-up




Add_half Module

 

```
module Add_half(c_out, sum, a, b);  
  output sum, c_out;  
  input a, b;  
  
  xor sum_bit(sum, a, b);  
  and carry_bit(c_out, a, b);  
endmodule
```

Add_full Module

 

```
module Add_full(c_out, sum, a, b, c_in) ;  
    output sum, c_out;  
    input a, b, c_in;  
    wire w1, w2, w3;  
  
    Add_half AH1(.sum(w1), .c_out(w2), .a(a), .b(b));  
    Add_half AH2(.sum(sum), .c_out(w3), .a(c_in), .b(w1));  
    or carry_bit(c_out, w2, w3);  
endmodule
```

Can Mix Styles In Hierarchy!

```
module Add_half_bhv(c_out, sum, a, b);  
  output reg sum, c_out;  
  input a, b;  
  always @(a, b) begin  
    sum = a ^ b;  
    c_out = a & b;  
  end  
endmodule
```

```
module Add_full_mix(c_out, sum, a, b, c_in) ;  
  output sum, c_out;  
  input a, b, c_in;  
  wire w1, w2, w3;  
  Add_half_bhv AH1(.sum(w1), .c_out(w2),  
                    .a(a), .b(b));  
  Add_half_bhv AH2(.sum(sum), .c_out(w3),  
                    .a(c_in), .b(w1));  
  assign c_out = w2 | w3;  
endmodule
```

Hierarchy And Scope

- Parent cannot access “internal” signals of child
- If you need a signal, must make a port!

Example:

Detecting overflow

Overflow =

cout XOR cout6



Must output

overflow or cout6!

```
module add8bit(cout, sum, a, b);  
    output [7:0] sum;  
    output cout;  
    input [7:0] a, b;  
    wire cout0, cout1,... cout6;  
    FA A0(cout0, sum[0], a[0], b[0], 1'b0);  
    FA A1(cout1, sum[1], a[1], b[1], cout0);  
    ...  
    FA A7(cout, sum[7], a[7], b[7], cout6);  
endmodule
```

Hierarchy And Source Code

  - Can have all modules in a single file
 - Module order doesn't matter!
 - Good for small designs
 - Not so good for bigger ones
 - Not so good for module reuse (cut & paste)
- Can break up modules into multiple files
 - Helps with organization
 - Lets you find a specific module easily
 - Good for module reuse (add file to project)



Structural Verilog: Connections

- Positional or Connect by reference
 - Can be okay in some situations
 - ✓ Designs with very few ports
 - ✓ Interchangeable input ports (and/or/xor gate inputs)
 - Gets confusing for large #s of ports

```
module dec_2_4_en (A, E_n, D);
```

```
input [1:0] A;  
input E_n;  
output [3:0] D;  
.  
.  
.
```

```
wire [1:0] X;
```

```
wire W_n;
```

```
wire [3:0] word;
```

```
// instantiate decoder
```

```
dec_2_4_en DX (X, W_n, word);
```

Partial code instatiating decoder

Structural Verilog: Connections

- Explicit or Connect by name method
 - Helps avoid “misconnections”
 - Don’t have to remember port order
 - Can be easier to read
 - .<port name>(<signal name>)

```
module dec_2_4_en (A, E_n, D);
```

```
input [1:0] A;
```

```
input E_n;
```

```
output [3:0] D;
```

```
  .  
  .  
  .
```

```
wire [1:0] X;
```

```
wire W_n;
```

```
wire [3:0] word;
```

```
// instantiate decoder
```

```
dec_2_4_en DX (.A(X), .E_n(W_n),  
              .D(word));
```

Partial code instatiating decoder

Empty Port Connections

- Example: `module dec_2_4_en(A, E_n, D);`
 - `dec_2_4_en DX (X[1:0], , word);` // E_n is high impedance (z)
 - `dec_2_4_en DX (X[1:0], W_n ,);` // Outputs D[3:0] unused.
- General rules
 - Empty input ports => high impedance state (z)
 - Empty output ports => output not used
- Specify all input ports anyway!
 - Z as an input is very bad...why?
- Helps if no connection to output port name but leave empty:
 - `dec_2_4_en DX(.A(X[3:2]), .E_n(W_n), .D());`

Module Port List

- Multiple ways to declare the ports of a module

```
module Add_half(c_out, sum, a, b);  
    output sum, c_out;  
    input a, b;  
    ...  
endmodule
```

```
module Add_half(output c_out, sum,  
                input a, b);  
    ...  
endmodule
```

Module Port List

- Multiple ways to declare the ports of a module (example2)

```
module xor_8bit(out, a, b);  
    output [7:0] out;  
    input [7:0] a, b;  
    ...  
endmodule
```

```
module xor_8bit(output [7:0] out, input [7:0] a, b);  
    ...  
endmodule
```

Why Know Structural Verilog?

- Code you write to be synthesized will almost all be dataflow or behavioral
- You will write your test bench primarily in behavioral
- What needs structural Verilog?
 - Building hierarchy (instantiating blocks to form higher level functional blocks)
 - There are somethings you can't trust to synthesis, and need to instantiate library gates structurally and use *'don't touch'* directives for synthesis.
 - ✓ Intentional clock gating
 - ✓ Cross coupled SR latches (used when part of core goes to sleep)
 - Synthesis tools output structural verilog (gate level netlist). You need to be able to read this output.


Timing Controls For Simulation

- Can put “delays” in a Verilog design
 - Gates, wires, & behavioral statements
- Delays are useful for Simulation only!
 - Used to approximate “real” operation while simulating
 - Used to control testbench
- SYNTHESIS
 - Synthesis tool IGNORES these timing controls
 - ✓ Cannot tell a gate to wait 1.5 nanoseconds
 - ✓ Delay is a result of physical properties
 - Only timing (easily) controlled is on clock-cycle basis
 - ✓ Can tell synthesizer to attempt to meet cycle-time restriction

Zero Delay vs. Unit Delay

- When no timing controls specified: zero delay
 - Unrealistic – even electrons take time to move
 - OUT is updated same time A and/or B change:
and $A0(OUT, A, B)$
- Unit delay often used
 - Not accurate either, but closer...
 - “Depth” of circuit does affect speed!
 - Easier to see how changes propagate through circuit
 - OUT is updated 1 “unit” after A and/or B change:
and #1 $A0(OUT, A, B);$

Zero/Unit Delay Example

 

*Zero Delay:
Y and Z change
at same "time"
as A, B, and C!*

*Unit Delay:
Y changes 1 unit
after B, C*

*Unit Delay:
Z changes 1 unit
after A, Y*

Zero Delay					
T	A	B	C	Y	Z
0	0	0	0	0	0
1	0	0	1	0	0
2	0	1	0	0	0
3	0	1	1	1	1
4	1	0	0	0	1
5	1	0	1	0	1
6	1	1	0	0	1
7	1	1	1	1	1
8	0	0	0	0	0
9	0	0	1	0	0
10	0	1	0	0	0
11	0	1	1	1	1
12	1	0	0	0	1
13	1	0	1	0	1
14	1	1	0	0	1
15	1	1	1	0	1

Unit Delay					
T	A	B	C	Y	Z
0	0	1	0	x	x
1	0	1	0	0	x
2	0	1	0	0	0
3	0	1	1	0	0
4	0	1	1	1	0
5	0	1	1	1	1
6	1	0	0	1	1
7	1	0	0	0	1
8	1	1	1	0	1
9	1	1	1	1	1
10	1	0	0	1	1
11	1	0	0	0	1
12	0	1	0	0	1
13	0	1	0	0	0
14	0	1	1	0	0
15	0	1	1	1	0
16	0	1	1	1	1

Slide taken direct from Prof. Schulte


Types Of Delays

- Inertial Delay (Gates)
 - Suppresses pulses shorter than delay amount
 - In reality, gates need to have inputs held a certain time before output is accurate
 - This models that behavior
- Transport Delay (Nets)
 - “Time of flight” from source to sink
 - Short pulses transmitted
- Not critical for our project, however, in industry
 - After APR an SDF is applied for accurate simulation
 - Then corner simulations are run to ensure design robust


Delay Examples

- `wire #5 net_1;` // 5 unit transport delay
- `and #4 (z_out, x_in, y_in);` // 4 unit inertial delay
- `assign #3 z_out = a & b;` // 3 unit inertial delay
- `wire #2 z_out;` // 2 unit transport delay
- `and #3 (z_out, x_in, y_in);` // 3 for gate, 2 for wire
- `wire #3 c;` // 3 unit transport delay
- `assign #5 c = a & b;` // 5 for assign, 3 for wire


Combinational Logic will Generate Pulses

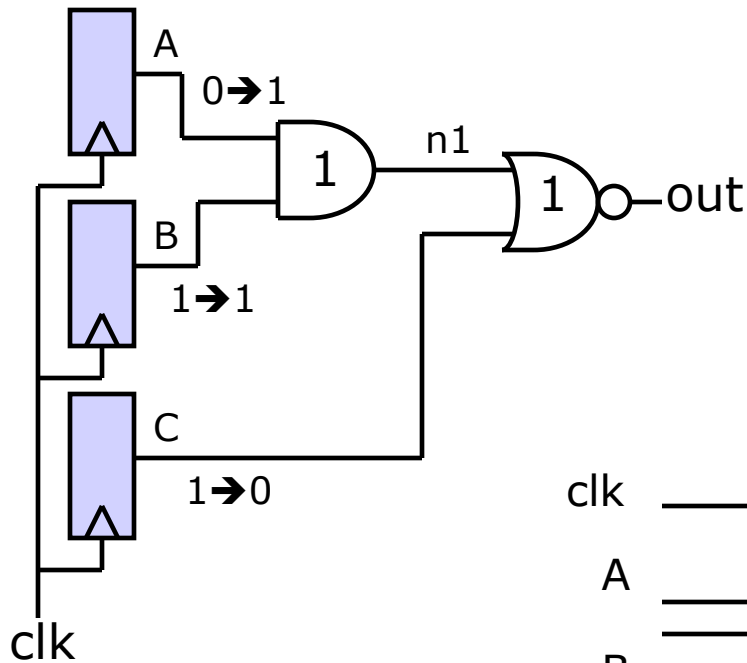

 - Have 3 Flops with a unit delay clk2q
- Feeds simple combinational logic with unit gate delays
- A,B,C make the transitions shown
- What does "out" do?



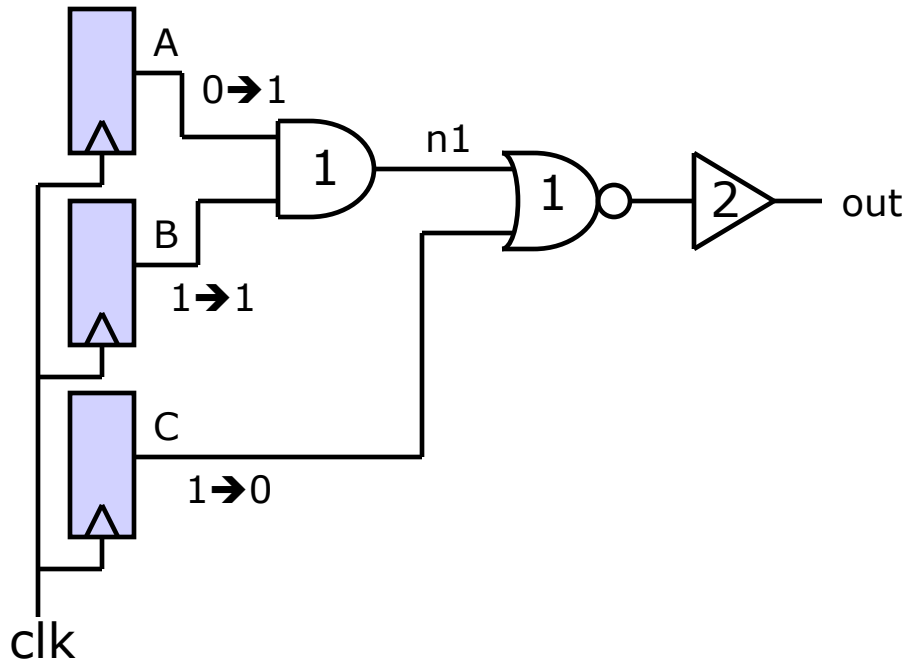Inertial Delay (tries to model gate delay)





- If we add a buffer with a 2 unit delay to the end of this circuit, now what happens?


- Remember the inertial gate delay will filter any pulse shorter than the specified delay...The pulse is eaten.

Gate Delay Variation (Verilog Handles This)

  - Gates don't have same delay in a rising transition vs falling
- Gates delays are not constant
 - Vary with PVT (Process, Voltage, Temperature)
 - You will hear reference to PVT corners
 - ✓ (fff,typ,sss) = (min,typ,max)




Rise/Fall/Turn Off

 

Referenced to
what the output
of the gate is
doing
 
`not #(2,1) inv1(out,in);` // not gate with 2 unit rise and 1 unit fall



Turn Off delay =
Time from cntrl to
high impedance

`bufif1 #(1,1,2) tri1(out,in,en);` // tri-state gate with unit rise/fall and 2 unit off

Min/Typ/Max Delay

- Speed, Speed, Speed
 - If you need to ensure speed of your circuit you want to perform your worst case analysis with the longest (max) delays.

- Perhaps more dangerous is a min-delay case. Race condition. If circuit has a race that is not met, it will fail at any clock speed.
 - To ensure your circuit is immune to race conditions (i.e. clock skew) you want to perform your worst case analysis with shortest (min) delays.

Min/Typ/Max

- Verilog supports different timing sets.

and #(1:2:3) g1(out,a,b); // 1 ns min, 2ns typical, 3ns max delay

- Can specify min/typ/max for rise and fall separate)

and #(2:3:4, 1:2:3) g1(out,a,b); // gate has different rise,fall for min:typ:max

- Selection of timing set can is typically done in simulation environment

% verilog test.v +maxdelays

Invoke command line verilog engine (like Verilog XL) selecting the maxdelay time set.

Design Flow

