

HW 11 – Universal counter

Verilog

```
module univ_bin_counter
#(parameter N = 8)
(
    input wire clk, reset,
    input wire syn_clr, load, en, up,
    input wire [N-1:0] d,
    output wire max_tick, min_tick,
    output wire [N-1:0] q
);

    // signal declaration
    reg [N-1:0] r_reg, r_next;

    // register
    always @(posedge clk, posedge reset)
    if(reset)
        r_reg <= 0;
    else r_reg <= r_next;

    // next-state logic
    always @*
    if (syn_clr)
        r_next = 0;
    else if (load)
        r_next = d;
    else if (en & up)
        r_next = r_reg + 1;
    else if (en & ~up)
        r_next = r_reg - 1;
    else
        r_next = r_reg;

    // Output
    assign q = r_reg;
    assign max_tick = (r_reg == 2**N-1) ? 1'b1 : 1'b0;
    assign min_tick = (r_reg == 0) ? 1'b1 : 1'b0;
endmodule
```

Testbench

```
`timescale 1ns/10ps
```

```
module bin_counter_tb();
```

```
    localparam T = 20; //clock period
```

```
    reg clk, reset;
```

```
    reg syn_clr, load, en, up;
```

```
    reg [2:0] d;
```

```
    wire max_tick, min_tick;
```

```
    wire [2:0] q;
```

```
univ_bin_counter #(.N(3)) uut
(.clk(clk),
.reset(reset),
.syn_clr(syn_clr),
.load(load),
.en(en),
.up(up),
.d(d),
.max_tick(max_tick),
.min_tick(min_tick),
.q(q));
```

```
always
```

```
begin
```

```
clk = 1'b1;
```

```
 #(T/2);
```

```
clk = 1'b0;
```

```
 #(T/2);
```

```
end
```

```
initial
```

```
begin
```

```
reset = 1'b1;
```

```
 #(T/2);
```

```
reset = 1'b0;
```

```
end
```

```
//Other stimulus
```

```
initial
```

```
begin
```

```

// === initial input ===
syn_clr = 1'b0;
load = 1'b0;
en = 1'b0;
up = 1'b1;
d = 3'b000;

@(negedge reset);
@(negedge clk);

load = 1'b1;
d = 3'b011;
@(negedge clk);
load = 1'b0;
repeat (2) @(negedge clk);
// === Test syn_clr ===
syn_clr = 1'b1;
@(negedge clk);
syn_clr = 1'b0;
// == Test up counter and pause ==
en = 1'b1;
up = 1'b1;
repeat(10) @(negedge clk);
en = 1'b0;
repeat(2) @(negedge clk);
en = 1'b1;
repeat(2) @(negedge clk);

// === test down counter ===
up = 1'b0;
repeat(10) @(negedge clk);

```

```

// === wait statement ===

// continue till q = 2
wait (q ==2);

@(negedge clk);univ_bin_counter #(.N(3)) uut
(.clk(clk),
.reset(reset),
.syn_clr(syn_clr),
.load(load),
.en(en),
.up(up),
.d(d),
.max_tick(max_tick),
.min_tick(min_tick),
.q(q));

always
begin
clk = 1'b1;
#(T/2);
clk = 1'b0;
#(T/2);
end

initial
begin
reset = 1'b1;
#(T/2);
reset = 1'b0;
end

```

```
//Other stimulus

initial
begin
// === initial input ===

syn_clr = 1'b0;
load = 1'b0;
en = 1'b0;
up = 1'b1;
d = 3'b000;
@(negedge reset);
@(negedge clk);


load = 1'b1;
d = 3'b011;
@(negedge clk);
load = 1'b0;
repeat (2) @(negedge clk);
// === Test syn_clr ===
syn_clr = 1'b1;
@(negedge clk);
syn_clr = 1'b0;
// == Test up counter and pause ==
en = 1'b1;
up = 1'b1;
repeat(10) @(negedge clk);
en = 1'b0;
repeat(2) @(negedge clk);
en = 1'b1;
repeat(2) @(negedge clk);
```

```

// === test down counter ===

up = 1'b0;
repeat(10) @(negedge clk);

// === wait statement ===

up = 1'b1;
// continue until min_tick becomes 1
@(negedge clk);
wait(min_tick);
@(negedge clk);
up = 1'b0;
// === absolute delay ===
#(4*T);
en = 1'b0;
#(4*T);
$stop;
end


initial

$monitor($time, " clk=%b reset=%b syn_clr=%b load=%b en=%b up=%b d=%b q=%b min_tick=%b
max_tick=%b", clk, reset,syn_clr,load,en,up,d,q,min_tick,max_tick);

endmodule

Wave\

```

 

Results

```
# run -all
0 clk=1 reset=1 syn_clr=0 load=0 en=0 up=1 d=000 q=000 min_tick=1 max_tick=0
10 clk=0 reset=0 syn_clr=0 load=0 en=0 up=1 d=000 q=000 min_tick=1 max_tick=0
20 clk=1 reset=0 syn_clr=0 load=0 en=0 up=1 d=000 q=000 min_tick=1 max_tick=0
30 clk=0 reset=0 syn_clr=0 load=1 en=0 up=1 d=011 q=000 min_tick=1 max_tick=0
40 clk=1 reset=0 syn_clr=0 load=1 en=0 up=1 d=011 q=011 min_tick=0 max_tick=0
50 clk=0 reset=0 syn_clr=0 load=0 en=0 up=1 d=011 q=011 min_tick=0 max_tick=0
60 clk=1 reset=0 syn_clr=0 load=0 en=0 up=1 d=011 q=011 min_tick=0 max_tick=0
70 clk=0 reset=0 syn_clr=0 load=0 en=0 up=1 d=011 q=011 min_tick=0 max_tick=0
80 clk=1 reset=0 syn_clr=0 load=0 en=0 up=1 d=011 q=011 min_tick=0 max_tick=0
90 clk=0 reset=0 syn_clr=1 load=0 en=0 up=1 d=011 q=011 min_tick=0 max_tick=0
100 clk=1 reset=0 syn_clr=1 load=0 en=0 up=1 d=011 q=000 min_tick=1 max_tick=0
110 clk=0 reset=0 syn_clr=0 load=0 en=1 up=1 d=011 q=000 min_tick=1 max_tick=0
120 clk=1 reset=0 syn_clr=0 load=0 en=1 up=1 d=011 q=001 min_tick=0 max_tick=0
130 clk=0 reset=0 syn_clr=0 load=0 en=1 up=1 d=011 q=001 min_tick=0 max_tick=0
140 clk=1 reset=0 syn_clr=0 load=0 en=1 up=1 d=011 q=010 min_tick=0 max_tick=0
150 clk=0 reset=0 syn_clr=0 load=0 en=1 up=1 d=011 q=010 min_tick=0 max_tick=0
160 clk=1 reset=0 syn_clr=0 load=0 en=1 up=1 d=011 q=011 min_tick=0 max_tick=0
170 clk=0 reset=0 syn_clr=0 load=0 en=1 up=1 d=011 q=011 min_tick=0 max_tick=0
180 clk=1 reset=0 syn_clr=0 load=0 en=1 up=1 d=011 q=100 min_tick=0 max_tick=0
190 clk=0 reset=0 syn_clr=0 load=0 en=1 up=1 d=011 q=100 min_tick=0 max_tick=0
200 clk=1 reset=0 syn_clr=0 load=0 en=1 up=1 d=011 q=101 min_tick=0 max_tick=0
210 clk=0 reset=0 syn_clr=0 load=0 en=1 up=1 d=011 q=101 min_tick=0 max_tick=0
220 clk=1 reset=0 syn_clr=0 load=0 en=1 up=1 d=011 q=110 min_tick=0 max_tick=0
230 clk=0 reset=0 syn_clr=0 load=0 en=1 up=1 d=011 q=110 min_tick=0 max_tick=0
240 clk=1 reset=0 syn_clr=0 load=0 en=1 up=1 d=011 q=111 min_tick=0 max_tick=1
250 clk=0 reset=0 syn_clr=0 load=0 en=1 up=1 d=011 q=111 min_tick=0 max_tick=1
260 clk=1 reset=0 syn_clr=0 load=0 en=1 up=1 d=011 q=000 min_tick=1 max_tick=0
270 clk=0 reset=0 syn_clr=0 load=0 en=1 up=1 d=011 q=000 min_tick=1 max_tick=0
280 clk=1 reset=0 syn_clr=0 load=0 en=1 up=1 d=011 q=001 min_tick=0 max_tick=0
290 clk=0 reset=0 syn_clr=0 load=0 en=1 up=1 d=011 q=001 min_tick=0 max_tick=0
300 clk=1 reset=0 syn_clr=0 load=0 en=1 up=1 d=011 q=010 min_tick=0 max_tick=0
310 clk=0 reset=0 syn_clr=0 load=0 en=0 up=1 d=011 q=010 min_tick=0 max_tick=0
320 clk=1 reset=0 syn_clr=0 load=0 en=0 up=1 d=011 q=010 min_tick=0 max_tick=0
330 clk=0 reset=0 syn_clr=0 load=0 en=0 up=1 d=011 q=010 min_tick=0 max_tick=0
340 clk=1 reset=0 syn_clr=0 load=0 en=0 up=1 d=011 q=010 min_tick=0 max_tick=0
350 clk=0 reset=0 syn_clr=0 load=0 en=1 up=1 d=011 q=010 min_tick=0 max_tick=0
360 clk=1 reset=0 syn_clr=0 load=0 en=1 up=1 d=011 q=011 min_tick=0 max_tick=0
370 clk=0 reset=0 syn_clr=0 load=0 en=1 up=1 d=011 q=011 min_tick=0 max_tick=0
380 clk=1 reset=0 syn_clr=0 load=0 en=1 up=1 d=011 q=100 min_tick=0 max_tick=0
390 clk=0 reset=0 syn_clr=0 load=0 en=1 up=0 d=011 q=100 min_tick=0 max_tick=0
400 clk=1 reset=0 syn_clr=0 load=0 en=1 up=0 d=011 q=011 min_tick=0 max_tick=0
410 clk=1 reset=0 syn_clr=0 load=0 en=1 up=0 d=011 q=011 min_tick=0 max_tick=0
```

Web coverage report

TestplanDesignDesUnits

bin_counter_tb

Number of tests run:1

Passed:1

Warning:0

Error:0

Fatal:0

List of tests included in report...

List of global attributes included in report...

List of Design Units included in report...

Coverage Summary by Structure:

Design Scope	Hits %	Coverage %
bin_counter_tb	91.53%	91.55%
unit	90.62%	92.50%

Coverage Summary by Type:

Total Coverage:						91.53%	91.55%
Coverage Type	Bins	Hits	Misses	Weight	% Hit	Coverage	
Statements	59	59	0	1	100.00%	100.00%	
Branches	7	7	0	1	100.00%	100.00%	
FEC Expressions	2	2	0	1	100.00%	100.00%	
FEC Conditions	4	3	1	1	75.00%	75.00%	
Toggles	58	48	10	1	82.75%	82.75%	

Report generated by ModelSim (ver. 10.7) on Monday 26 December 2022 10:23:13 with command line:
vccover report -html uni_counter.ucdb