

## ASSIGNMENT WEEK 4:

### STRUCTURAL MODEL AND TESTBENCH BASICS

#### Problem 1. 16 – bit Carry Look Ahead Adder

Write code Verilog: Design code and testbench code.


*Note: A 16 – bit Carry Look Ahead Adder can be formed by cascading four 4 – bit Carry Look Ahead Adder.*

#### Problem 2. Ripple Carry Counter

Write code Verilog: Design code and testbench code for Ripple Carry Counter

Simulate and explain your design.

 *Note: Using T - flipflop (structural model) you designed in week 3.*



#### Problem 3. Design 4 – bit Gray Counter.

Write code Verilog: Design code and simulation by testbench.

*Note: Using \$display syntax and screenshot waveform.*

#### Problem 4. Design BCD to 7 Segment Display Decoder.

Write code Verilog: Design code and simulation by testbench.

