

# ET5080E

# Digital Design Using Verilog HDL

---

Fall '21

Simulator Mechanics

Testbench Basics (stimulus generation)

Dataflow Verilog

# Administrative Matters

---

- Readings
  - Text Chapter 6 (*Dataflow Verilog, vector concatenation, operators*)
- Synthesis Tutorial coming in couple of weeks
- HW2 assigned...posted



# Analog Simulation (Spice Engine)

---



- Divide “time” into slices
- Update information in whole circuit at each slice
- Used by SPICE
- Allows detailed modeling of current and voltage
- Computationally intensive and slow
- Don't need this level of detail for most digital logic simulation
  
# Digital Simulation

- Could update every signal on an input change



  
- Could update just the full path on input change



- Don't even need to do that much work!

# Event-Driven Simulation



---

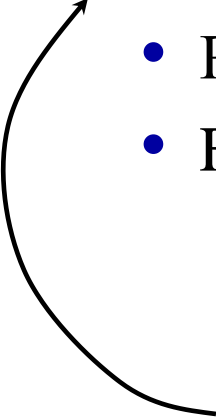- When an input to the simulating circuit changes, put it on a “changed” list
  - Loop while the “changed” list isn’t empty:
    - Remove a signal from the “changed” list
    - For each sink of the signal
      - ✓ Recompute its new output(s)
      - ✓ For any output(s) that have changed value, add that signal to the “changed” list
  - When the “changed” list is empty:
    - Keep simulation results
    - Advance simulation time to next stimulus (input) event
- 

# Simulation

---


- Update only if changed

  


- Some circuits are very large
  - Updating every signal => very slow simulation
  - Event-driven simulation is much faster!
 
# Testbench Basics (stimulus generation)


- Need to verify your design
  - “Design Under Test” (DUT)
- Use a “testbench”
  - Special Verilog module with no ports
  - Generates or routes inputs to the DUT
  - For now we will monitor outputs via human interface



OR

 


# Simulation Example

 

Our DUT is a simple 4-bit adder, with carry in and carry out

Use a consistent naming convention for your test benches:

 I usually add `_tb` to the end of the unit name



***adder4bit\_tb***



# Testbench Requirements

---

- Instantiate the unit being tested (DUT)
- Provide input to that unit
  - Usually a number of different input combinations!
- Watch the “results” (outputs of DUT)
  - Can watch ModelSim Wave window...
  - Can print out information to the screen or to a file
- This way of monitoring outputs (human interface) is dangerous & incomplete.
  - Subject to human error
  - Cannot be automated into batch jobs (regression suite)
  - Self checking testbenches will be covered later

# Output Test Info

---

- Several different system calls to output info
  - \$monitor
    - ✓ Output the given values whenever one changes
    - ✓ Can use when simulating Structural, RTL, and/or Behavioral
  - \$display, \$strobe
    - ✓ Output specific information like a `printf` in a C program
    - ✓ Used in Behavioral Verilog
- Can use formatting strings with these commands
- Only means anything in simulation
- Ignored by synthesizer

# Output Format Strings

---

- Formatting string
  - %h, %H            hex
  - %d, %D            decimal
  - %o, %O            octal
  - %b, %B            binary
  - %t                            time
- `$monitor(“%t: %b %h %h %h %b\n”,  
                          $time, c_out, sum, a, b, c_in);`
- Can get more details from Verilog standard

# Output Example

```
module adder4bit_tb;  
  reg[8:0] stim;  
  wire[3:0] S;  
  wire C4;  
  
  // instantiate DUT  
  adder4bit(.sum(S), .c_out(C4), .a(stim[8:5]), .b(stim[4:1]), .c(stim[0]));  
  
  initial $monitor("%t A:%h B:%h ci:%b Sum:%h co:%b\n", $time,  
                  stim[8:5], stim[4:1], stim[0], C4, S);  
  
  // stimulus generation  
  initial begin  
    stim = 9'b0000_0000_0;      // at 0 ns  
    #10 stim = 9'b1111_0000_1;  // at 10 ns  
    #10 stim = 9'b0000_1111_1;  // at 20 ns  
    #10 stim = 9'b1111_0001_0;  // at 30 ns  
    #10 stim = 9'b0001_1111_0;  // at 40 ns  
    #10 $stop;                  // at 50 ns – stops simulation  
  
  end  
endmodule
```

# Exhaustive Testing

---

- For combinational designs w/ up to 8 or 9 inputs
  - Test ALL combinations of inputs to verify output
  - Could enumerate all test vectors, but don't...
  - Generate them using a “for” loop!

```
reg [4:0] x;  
initial begin  
    for (x = 0; x < 16; x = x + 1)  
        #5;    // need a delay here!  
end
```

- Need to use “reg” type for loop variable? Why?

# Why Loop Vector Has Extra Bit

---

- Want to test all vectors 0000 to 1111

```
reg [3:0] x;
```

```
initial begin
```

```
    for (x = 0; x < 16; x = x + 1)
```

```
        #5; // need a delay here!
```

```
end
```

- If x is 4 bits, it only gets up to 1111 => 15
  - 1100 => 1101 => 1110 => 1111 => 0000 => 0001
- x is never  $\geq 16$ ... so loop goes forever

# Example: DUT

---

```
module Comp_4 (A_gt_B, A_lt_B, A_eq_B, A, B);  
output A_gt_B, A_lt_B, A_eq_B;  
input   [3:0] A, B;  
    // Code to compare A to B  
    // and set A_gt_B, A_lt_B, A_eq_B accordingly  
endmodule
```

# Example: Testbench

```
module Comp_4_tb();  
wire    A_gt_B, A_lt_B, A_eq_B;  
reg     [4:0] A, B;                                // sized to prevent loop wrap around  
  
Comp_4 M1 (A_gt_B, A_lt_B, A_eq_B, A[3:0], B[3:0]);    // DUT  
  
initial $monitor("%t A: %h B: %h AgtB: %b AltB: %b AeqB: %b",  
    $time, A[3:0], B[3:0], A_gt_B, A_lt_B, A_eq_B);  
initial #2000 $finish;                                // end simulation, quit program  
  
initial begin  
#5 for (A = 0; A < 16; A = A + 1) begin                // exhaustive test of valid  
    inputs  
    for (B = 0; B < 16; B = B + 1) begin #5; // may want to test x's and z's  
    end // first for  
    end // second for  
end // initial  
endmodule
```


*note multiple  
initial blocks*


 
# Do ModelSim Example Here

---

- ModelSim Example of 3-bit wide adder block



# Combinational Testbench

```
module comb(output d, e, input a, b, c);  
  and(d, a, b);  
  nor(e, a, b, c);  
endmodule
```

Does exhaustively testing a simple combinational block made with Verilog primitives make sense?

```
module comb_tb();  
  wire      d, e;  
  reg [3:0] abc;  
  
  comb CMD(.d(d),.e(e), .a(abc[2]), .b(abc[1]), .c(abc[0])); // DUT  
  
  initial $monitor("%t a: %b b: %b c: %b d: %b e: %b", $time,  
    abc[2], abc[1], abc[0], d, e);  
  initial #2000 $finish;           // end simulation, quit program  
  
  // exhaustive test of valid inputs  
  initial begin  
    for (abc = 0; abc < 8; abc = abc + 1) #5;  
  end // initial  
endmodule
```

# Generating Clocks

---

- Wrong way:

```
initial begin  
    #5 clk = 0;  
    #5 clk = 1;  
    #5 clk = 0;  
    ... (repeat hundreds of times)  
end
```

- Right way:

```
initial clk = 0;  
always @(clk) clk = #5 ~clk;
```

```
✓ initial begin  
    clk = 0;  
    forever #5 clk = ~clk;  
end
```

- LESS TYPING

- Easier to read, harder to make mistake

# FSM Testing

---

- Response to input vector depends on state
- For each state:
  - Check all transitions
  - For Moore, check output at each state
  - For Mealy, check output for each transition
  - This includes any transitions back to same state!
- Can be time consuming to traverse FSM repeatedly...

# Example : Gray Code Counter – Test1 *(the instructor is a chicken)*

---

- Write a testbench to test a gray code counter  
**module** gray\_counter(out, clk, rst);
- Rst in this case is a synchronous reset
  - It does not directly asynchronously reset the flops
  - It is an input to the combinational logic that sets the next state to all 0's.
- Initially reset the counter and then test all states, but do not test reset in each state.

# Solution : Gray Code Counter – Test1

---

```
module t1_gray_counter();  
  wire [2:0] out;  
  reg clk, rst;  
  gray_counter GC(out, clk, rst); // DUT  
  
  initial $monitor("%t out: %b rst: %b ", $time, out, rst); // no  
  clock  
  initial #100 $finish; // end simulation, quit program  
  
  initial begin  
    clk = 0; forever #5 clk = ~clk; // What is the clock period?  
  end  
  initial begin  
    rst = 1; #10 rst = 0; // just reset and let it run  
  end // initial  
endmodule
```

# Simulation: Gray Code Counter – Test1

---

```
#          0 out: xxx rst: 1          // reset system
#          5 out: 000 rst: 1          // first positive edge
#         10 out: 000 rst: 0          // release reset
#         15 out: 001 rst: 0          // traverse states
#         25 out: 011 rst: 0
#         35 out: 010 rst: 0
#         45 out: 110 rst: 0
#         55 out: 111 rst: 0
#         65 out: 101 rst: 0
#         75 out: 100 rst: 0
#         85 out: 000 rst: 0
#         95 out: 001 rst: 0
```

# Force/Release In Testbenches

---

- Allows you to “override” value FOR SIMULATION
- Doesn’t do anything in “real life”
- How does this help testing?
  - Can help to pinpoint bug
  - Can use with FSMs to override state
    - ✓ Force to a state
    - ✓ Test all edges/outputs for that state
    - ✓ Force the next state to be tested, and repeat
- Can help achieve code coverage (*more on that later*)



# Force/Release Example

---

```
assign y = a & b;  
assign z = y | c;  
initial begin  
    a = 0; b = 0; c = 0;  
    #5 a = 0; b = 1; c = 0;  
    #5 force y = 1;  
    #5 b = 0;  
    #5 release y;  
    #5 $stop;  
end
```

<b>T</b>	<b>a</b>	<b>b</b>	<b>c</b>	<b>y</b>	<b>z</b>
<b>0</b>	0	0	0	0	0
<b>5</b>	0	1	0	0	0
<b>10</b>	0	1	0	1	1
<b>15</b>	0	0	0	1	1
<b>20</b>	0	0	0	0	0

# Example : Gray Code Counter – Test2

---

- Write a testbench to exhaustively test the gray code counter example above  
**module** gray\_counter(out, clk, rst);
- Initially reset the counter and then test all states, then test reset in each state.
- Remember that in this example, rst is treated as an input to the combinational logic.

# Example : Gray Code Counter – Test2

```
module t2_gray_counter();  
  wire [2:0] out;  
  reg   clk, rst;  
  gray_counter GC(out, clk, rst); // DUT
```

**Note** the Use of hierarchical Naming to get at the internal Signals. This is a very handy Thing in testbenches.

```
  initial $monitor("%t out: %b rst: %b ", $time, out, rst); // no clock  
  initial #300 $finish;           // end simulation, quit program
```

```
  initial begin
```

```
    clk = 0; forever #5 clk = ~clk; // What is the clock period?
```

```
  end
```

```
  initial begin
```

```
    rst = 1; #10 rst = 0;
```

```
    #90 rst = 1; force GC.ns = 3'b001; #10 release GC.ns;
```

```
    #10 force GC.ns = 3'b011; #10 release GC.ns;
```

```
    #10 force GC.ns = 3'b010; #10 release GC.ns;
```

```
    ...
```

```
  end // initial
```

```
endmodule
```

# Simulation: Gray Code Counter – Test2

---

# 0 out: xxx rst: 1	# 100 out: 001 rst: 1	# 215 out: 000 rst: 1
# 5 out: 000 rst: 1	# 105 out: 000 rst: 1	# 225 out: 101 rst: 1
# 10 out: 000 rst: 0	// at #115 out = 000	# 235 out: 000 rst: 1
# 15 out: 001 rst: 0	# 125 out: 001 rst: 1	# 245 out: 100 rst: 1
# 25 out: 011 rst: 0	# 135 out: 000 rst: 1	# 255 out: 000 rst: 1
# 35 out: 010 rst: 0	# 145 out: 011 rst: 1	
# 45 out: 110 rst: 0	# 155 out: 000 rst: 1	
# 55 out: 111 rst: 0	# 165 out: 010 rst: 1	
# 65 out: 101 rst: 0	# 175 out: 000 rst: 1	
# 75 out: 100 rst: 0	# 185 out: 110 rst: 1	
# 85 out: 000 rst: 0	# 195 out: 000 rst: 1	
# 95 out: 001 rst: 0	# 205 out: 111 rst: 1	

# Dataflow Verilog

---

- The continuous **assign** statement
  - It is the main construct of Dataflow Verilog
  - It is deceptively powerful & useful
- Generic form:

```
assign [drive_strength] [delay] list_of_net_assignments;
```

*Where:*

`list_of_net_assignment ::= net_assignment [{,net_assignment}]`

*& Where:*

*Net\_assignment ::= net\_lvalue = expression*

OK...that means just about nothing to me...how about some examples?

# Continuous Assign Examples

---

- Simplest form:

```
// out is a net, a & b are also nets  
assign out = a & b; // and gate functionality
```

- Using vectors

```
wire [15:0] result, src1, src2; // 3 16-bit wide vectors  
assign result = src1 ^ src2; // 16-bit wide XOR
```

- Can you implement a 32-bit adder in a single line?

```
wire [31:0] sum, src1, src2; // 3 32-bit wide vectors  
assign {c_out,sum} = src1 + src2 + c_in; // wow!
```

*What is this?*


# Vector concatenation

---

- Can “build” vectors using smaller vectors and/or scalar values
- Use the { } operator
- Example 1

```
module concatenate(out, a, b, c, d);  
  input [2:0] a;  
  input [1:0] b, c;  
  input d;  
  output [9:0] out;  
  
  assign out = {a[1:0],b,c,d,a[2]};  
  
endmodule
```

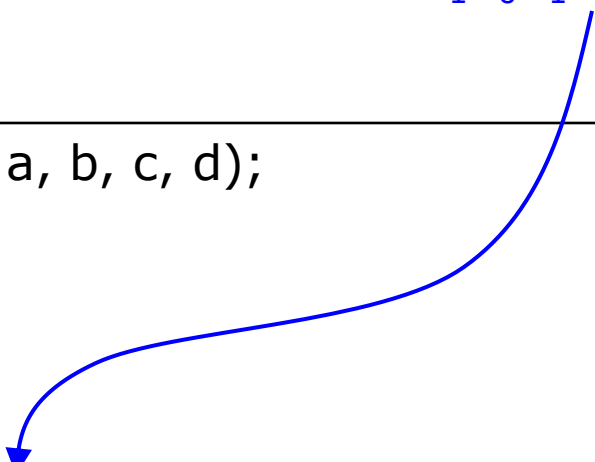*becomes  
8-bit vector:  
a<sub>1</sub>a<sub>0</sub>b<sub>1</sub>b<sub>0</sub>c<sub>1</sub>c<sub>0</sub>da<sub>2</sub>*




# Vector concatenation

---
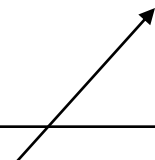
## ■ Example 2

```
module add_concatenate(out, a, b, c, d);  
    input [7:0] a;  
    input [4:0] b;  
    input [1:0] c;  
    input d;  
    output [7:0] out;  
  
    add8bit(.sum(out), .cout(), .a(a), .b({b,c,d}), .cin());  
  
endmodule
```



- Vector concatenation is not limited to assign statements. In this example it is done in a port connection of a module instantiation.



# Replication within Concatenation

---

- Sometimes it is useful to replicate a bit (or vector) within the concatenation of another vector.
  - This is done with a replication constant (number) in front of the { }
  - Example: (sign extend an 8-bit value to a 16bit bus)

```
input [7:0] offset; // 8-bit offset term from EEPROM


wire [15:0] src1,src2; // 16-bit source busses to ALU

assign src1 = {8{offset[7]},offset}; // sign extend offset term
```

- Recall, to sign extend a 2's complement number you just replicate the MSB.
  - In this example the MSB of the 8-bit offset term has to be replicated 8 times to flush out to a full 16-bit value

# Back to the Continuous Assign

- More basic generic form:  
    `assign <LHS> = <RHS expression>;`
- If RHS result changes, LHS is updated with new value
  - Constantly operating (“continuous”)
  - It's **hardware!**
  - RHS can use operators (i.e. +, -, &, |, ^, ~, >>, ...)

 

`assign {c_out,sum} = src1 + src2 + c_in;`

# Operators: Arithmetic

---

- Much easier than structural!

*	multiply	**	exponent
/	divide	%	modulus
+	add	-	subtract

- Some of these don't synthesis
- Also have unary operators +/- (pos/neg)
- Understand bitsize!
  - Can affect sign of result
  - Is affected by bitwidth of BOTH sides

$\text{Prod}[7:0] = a[3:0] * b[3:0]$

# Operators

---

- Shift (<<, >>, <<<, >>>)
- Relational (<, >, <=, >=)
- Equality (==, !=, ===, !==)
  - ===, !== test x's, z's! ONLY USE FOR SIMULATION!
- Logical Operators (&&, ||, !)
  - Build clause for if statement or conditional expression
  - Returns single bit values
- Bitwise Operators (&, |, ^, ~)
  - Applies bit-by-bit!
- Watch ~ vs !, | vs. ||, and & vs. &&

# Reduction Operators

---

- Reduction operators are reduce all the bits of a vector to a single bit by performing an operation across all bits.
  - Reduction AND
    - ✓ `assign all_ones = &accumulator;      // are all bits set?`
  - Reduction OR
    - ✓ `assign not_zero = |accumulator;      // are any bits set?`
  - Reduction XOR
    - ✓ `assign parity = ^data_out;      // even parity bit`

# Lets Kick up the Horse Power

---

- You thought a 32-bit adder in one line was powerful. Lets try a 32-bit MAC...

Design a multiply-accumulate (MAC) unit that computes

$$Z[31:0] = A[15:0] * B[15:0] + C[31:0]$$

It sets overflow to one, if the result cannot be represented using 32 bits.

```
module mac(output Z [31:0], output overflow,  
           input [15:0] A, B, input [31:0] C);
```

# Lets Kick up the Horse Power

```
module mac(output Z [31:0], output overflow,  
           input [15:0] A, B, input [31:0] C);  
    assign {overflow, Z} = A*B + C;  
endmodule
```

I am a brilliant genius. I am a HDL coder extraordinaire. I created a 32-bit MAC, and I did it in a single line.

assign {overflow, Z} = A\*B + C;

Oh my god,  
I've created a  
monster

Synopsys



# Conditional Operator


- This is a favorite!
  - The functionality of a 2:1 Mux
  - `assign out = conditional_expr ? true_expr : false_expr;`

Examples:

```
// a 2:1 mux  
assign out = select ? in0 : in1;
```

```
// tri-state bus  
assign src1 = rf2src1 ? Mem[addr1] : 16'hzzzz;
```
 
```
// Either true_expr or false_expr can also be a conditional operator  
// lets use this to build a 4:1 mux  
assign out = sel[1] ? (sel[0] ? in3 : in2) : (sel[0] ? in1 : in0);
```





# Conditional assign (continued)

Examples: (nesting of conditionals)

```
`define add 3'b000
`define and 3'b001
`define xor 3'b010
`define shift_l 3'b011
`define shift_r 3'b100
```

// an ALU capable of arithmetic, logical, shift, and zero

```
assign {cout,dst} = (op==`add)    ?    src1+src2+cin :
                    (op==`and)    ?    {1'b0,src1 & src2} :
                    (op==`xor)    ?    {1'b0,src1 ^ src2} :
                    (op==`shift_l) ?    {src1,cin} :
                    (op==`shift_r) ?    {src1[0],src1[15],src1[15:1]} :
                                         17'h00000;
```

This can be very confusing to read if not coded with proper formatting

# A Few Other Possibilities

---

- The implicit assign
  - Goes in the wire declaration  
**wire** [3:0] sum = a + b;
  - Can be a useful shortcut to make code succinct, but doesn't allow fancy LHS combos  
**assign** {cout, sum} = a + b + cin;
  - Personal choice
    - ✓ You are welcome to use it when appropriate (I never do)

# Latches with Continuous Assign


---

- What does the following statement imply/do?  
**assign** q\_out = enable ? data\_in : q\_out;
  - It acts as a latch. If enable is high new data goes to q\_out. Otherwise q\_out maintains its previous value.
  - Ask yourself...It that what I meant when I coded this?
  - It simulates fine...just like a latch


# Latches with Continuous Assign

```
assign q_out = enable ? data_in : q_out;
```

- How does it synthesize??

 

 Is the synthesizer smart enough to see this as a latch and pick a latch element from the standard cell library?



Or is it what you code is what you get? A combinational feedback loop. Still acts like a latch. Do you feel comfortable with this?